TALKING ELECTRONICS

A NEW MAGAZINE FOR EXPERIMENTERS

$1.20*
N.Z. $1.40

Issue No 2.

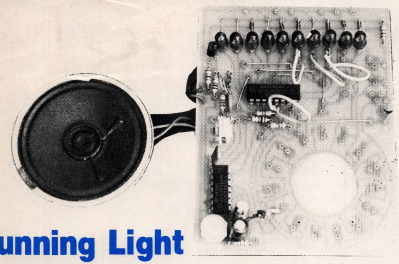

Running Light

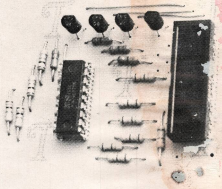

Counter Module

PRE-PAK catalogue INSIDE

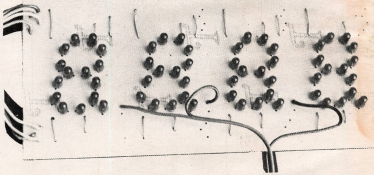

7- Segment Display

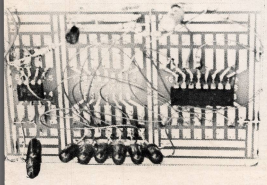

LED Dice

FREE! 2 TRANSISTORS!
See P.27 for details

Registered for posting as a publication – Category B

Save 25%

JUST RELEASED!

ELLISTRONICS

289 LATROBE ST., MELBOURNE 3000
602 3282 602 3836

3800A

$22.00
$25.30 inc tax

Max Input 10MHz
Memory/Pulse Sw.
TTL/CMOS Sw.
Input Impedance 300k
Smart black plastic case
53cm leads

2 NEW PROBES

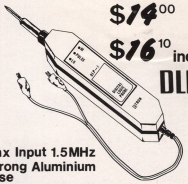

$14.00
$16.10 inc tax
DLP-1

Max Input 1.5MHz
Strong Aluminium case
LEDs: HI - LOW - PULSE
80cm leads
KEY to LEDs on back of probe
Input Impedance 300k

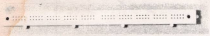

WB-DN 100 Holes
$1.98 $2.28 INC

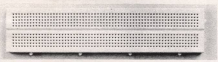

WB-TN 640 Holes
$7.57 $8.70 INC

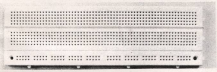

WB-2N-1 100 + 640 Holes
$9.65 $11.10 INC

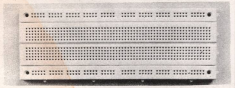

WB-2N 200 + 640 Holes
$11.21 $12.90 INC

NEW! BREAD BOARDS

Now DIRECTLY imported at ½ cost of other breadboards!

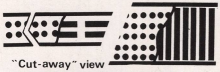

"Cut-away" view

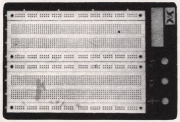

WB-4N 400 + 1280 Holes
$25.03 $28.78 INC

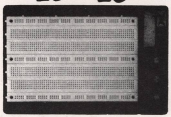

WB-4N-1 300+1280Holes
$23.50 $27.03 INC

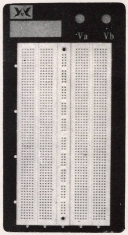

WB-4N-3 100+1280Holes
$19.59 $22.53 INC

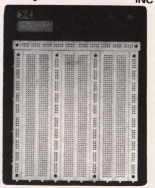

WB-6N 500+1920 Holes
$35.58 $40.92 INC

EACH ISSUE WILL FEATURE A PROJECT ON THESE BREAD BOARDS

CJ

SRD

TALKING ELECTRONICS

Vol.1 No.2

Editorial...

We derive a great deal of pleasure bringing out TALKING ELECTRONICS. The initial response has been very encouraging, so much so, our initial intention of a 32 page issue has exploded to 48 pages. From the letters it seems we have fulfilled a need in the experimenting field. We obviously have not satisfied it fully but at least have made a large dent. Many readers have requested we cover their pet interests such as computers, amplifiers, remote control, model railroad and CB radio.

For the moment we intend to concentrate on simple DIGITAL projects and provide a firm background to understanding this sector. We will also include an occasional article capable of fulfilling a dual role. Projects such as pocket transmitters, 4-amp power supplies, 20-watt stereo amplifiers for $5 and electronic traffic lights are in the pipe-line.

You can see the leaning has been towards instructional material with a back-up of questions to consolidate learning. This is our aim. We intend to lift the hobbyist who is new to electronics and gather in the more advanced with a series of graded articles. We can then extend our efforts to additional fields.

A key factor to positive learning is the tests and quizzes in each issue. These highlight the saying "You may know, but do you know you know?"

Colin Mitchell.

4	COUNTER MODULE
12	7-SEGMENT DISPLAY
15	AUST WIDE SUPPLIERS
19	BOX COMPARISONS
20	LED DICE
25	JUNIOR PUZZLE PAGE
26	PARTS LIST
27	SUB & ORDER FORMS
28	SHOP TALK
34	TV SERVICING
37	10 MINUTE DIGITAL COURSE
43	TEST YOURSELF Capacitors
44	TRICK SWITCH!
46	EXPERIMENTER DECK
50	QUIZ
51	PC BOARDS
52	DATA

Publisher

TALKING ELECTRONICS MAGAZINE is designed by Colin Mitchell with a great deal of help from Craig Jones in the technical drawing/designing department and Steven in the art department. Designed and Published at 35 Rosewarne Ave., Cheltenham, 3192. Suitable articles should be sent to this address where you will receive full assistance with final presentation. All material is copyright however up to 30 photocopies for clubs and schools is allowed. Bulk purchase may be cheaper than photocopying.

Printed Web offset by Std News @12,000 copies per hour!

Distributed in Australia by Gordon & Gotch.

*Maximum recommended retail price only.

COUNTER MODULE

— Craig Jones

Project cost: $19

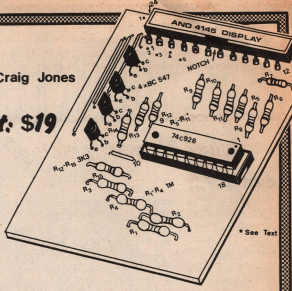

A counter is a very handy piece of equipment. It can be used as test equipment, for display, or for experimentation. Our versatile counter module is especially useful. Many variations and adaptions can be engineered around it, as it is a basic building block. It can be used to count from one cycle per hour to nearly 3MHz. To cater for frequencies higher than 3MHz, additional dividing networks can be included at the front end. This would extend the frequency 100 times or more.

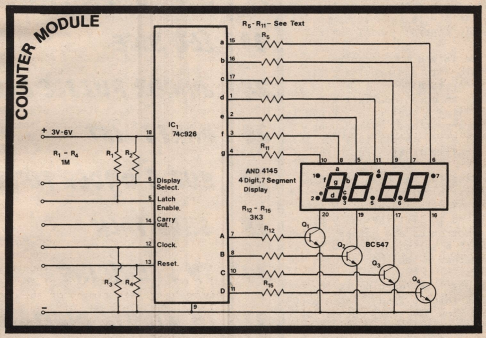

Our project will accept 6 different sensors; light, sound, magnetic, unit, oscillator, and infra-red.

Actually the counter module is quite an easy project. Most of the complexity is contained within the two chips and only a few outside components such as resistors need be added. These resistors interface (connect) between the counting chip and the display. They provide current limiting for the display segments and driver transistors. The four resistors at the input of the IC provide pull-up and pull-down. This sets the condition HIGH or LOW on the inputs as many have a dual role.

At first glance this project may seem expensive compared to a pocket calculator. Some calculators have unit-count facilities incorporated into the plus key and this can be extended externally to an oscillator or reed switch sensor. But a Calculator project doesn't give any constructional experience or enable you to add your own read-out. diagram. Nor does it allow you to add your own read-out.

Any of the six sensors can be fed into the 74C926. These will be the basis of the second part of this project. Consider this project as a paying proposition. You have been requested by an engineering firm to design a simple parts counter to tally daily production. Of course it is always possible to bulk-weigh components on a set of ratio-scales, but the management has stipulated an optical counter situated near the operator. You will be required to build a working proto-type for a four week trial-run. How do you think you will fair? The only catch is, you will have to wait for the next issue for the optical sensor.

Any manufacturing firm producing a number of similar items such as plastic parts, packaging of

small items, adding a label to a bottle or hand preparing or de-burring will find a unit-counting recorder of immense benefit. The main advantage of an electronic counter is the number of sensors it will accept. It's a very simple task to adapt optical, magnetic, or audio sensors to count production parts. And most importantly, it is the simplicity of set-up which will appeal to the operator.

What is multiplexing?

Our four digit "AND" display is multiplexed, but what does it mean?
It is a complex scanning process which we will discuss in a very simple way.
Looking into the display you will see it is capable of showing four figure "eights" and 7 decimal points. If you count up all the segments needed to make each eight, you will have (fill it in) plus 7 dots making a total of at least 35 LEDs. To operate this you would need at least 36 leads.
But the display has only 24 pins. How does that work? In fact 13 of the pins are connected directly to the dots, leaving only 11 pins for all the segments. Each digit has 7 segments, and you would normally assume you would need 4x7 or at least 28 or 29 pins to select any combination of the 28 segments and be able to display any number or letter. Under normal thinking you would be correct. However the technical boys have devised a method which joins the same segment in each digit with the next. This means all segments "a" are joined and all segments "b" are joined together etc. Again your reasoning would tell you that if a figure "eight" were to be presented as the first digit, then all the digits would show "eight". Correct. Now let us advance a little further. Instead of all the other ends (all the cathodes) of the 28 segments being connected together, we join the seven segments of each digit to a drive transistor making four separate items. This time, when the first digit shows a figure eight, we can choose which other digit becomes illuminated with an "eight" by turning on the relevant transistor.

To understand the next portion of our discussion you must change your whole thinking towards displays. They are not a static sign such as that outside a Milk Bar...they are living! They're like a miniature television screen. You know full well that a picture on a TV screen is made up of a single dot flying across the screen to produce 625 lines. And this is repeated 25 times per second. The dot is turned on and off to produce the black and white portions of the picture.
Our "AND" display can be thought of as a TV screen. The four drive transistors are turned on and off sequentially so that if a single segment of the first digit were illuminated, it would light briefly at the first digit then the second digit then the third and finally the fourth digit. In other words it would run the length of the display at about 25 times per second. Now your Persistence of Vision would interpret this as segment "a" in each digit being lit constantly. You cannot see flickering or jumping across the display beyond about 25 times per second.

Follow this experiment. Instead of supplying the display with energy all the time, we pulse it in synchronisation with the turning on and off of the third transistor. The result would be only segment "a" in the third digit lighting up. By using this method we can accurately pick out any segment of the 28 segment in the display. Try visualising how a top segment of digit three and a lower segment of the fourth digit can be selected with one passing of the scan. It merely requires accurate timing of the 7 pieces of information being fed into the display via pins 10,8,5,11,9,7 and 6 to coincide with the digit select transistors.

PIN OUTS:

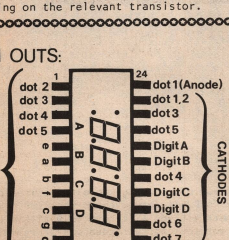

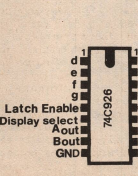

PARTS LIST:

IC1 - 74C926

Display - AND 4145

Resistors:

7 - 100R ¼W
7 - 180R "
7 - 220R "
7 - 270R "
7 - 330R "
Use ONLY ONE value SEE TEXT
4 - 3k3 "
4 - 1M "

4 - BC 547

1 - "COUNTER" PC board.

CHOOSING A DROPPER RESISTOR

To limit the current through each segment of the display we need 7 dropper resistors. The value of these resistors will be governed by the supply voltage. Once this is chosen you will be able to select a particular value of dropper resistor. A range of suitable resistors has been included in the kit of parts. You will not be needing all the resistors as some apply to a higher or lower voltage. They are not absolutely critical and a value either side of the one specified will operate quite satisfactorily. The only requirement is for the 7 resistors to be of the same value. Two or three different values will cause the display to be uneven. Fortunately the "AND" display is not quite so sensitive to slight voltage variations as it is constructed with Gallium Phosphide LED's which are a saturating type and produce a very even display somewhat independent of supply voltage.

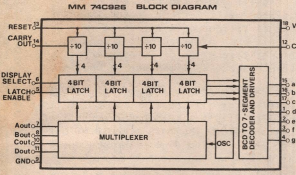

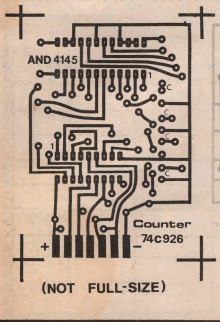

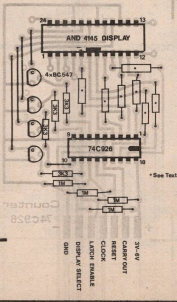

COUNTER FUNCTIONS:

DISPLAY SELECT:	HIGH - Display shows counter output. LOW - Display shows output of latch.
LATCH ENABLE:	HIGH:- Unlatched LOW - Latched
RESET:	HIGH - Resets to zero
CLOCK: counter counts on the negative edge.	
CARRY OUT: Goes HIGH at 5999/6000 LOW at 9999/0000	

Select the value of R_5 - R_{11} from this list:

SUPPLY VOLTAGE:	AND 4145
3v	7 - 100R
4.5v	7 - 220R
5v	7 - 270R
6v	7 - 330R
	HOME-MADE DISPLAY:
4.5v	7 - 100R
5v	7 - 180R
6v	7 - 270R

The 74C926 counter chip is capable of driving 4 digits. Refer to the block diagram for the sections contained within the chip.
The input frequency appears at the "clock" pin, number 12, and passes through 4 divide-by-ten counters. At each stage it emerges to be fed into a 4-bit latch. The outputs pass to a Binary-Coded-Decimal to 7 segment decoder and driver, where it feeds the display via dropper resistors.

The multiplexing network generates a set of synchronising pulses, one set feeding each of the 4 latches, the other set feeding A,B,C,Douts. The chip contains its own internal oscillator to drive the multiplex which in turn sets the scan rate for the display. This internal oscillator cannot be adjusted which is a pity really, it would be nice to lower the scan to a point where each of the 4 digits can be viewed turning on and off sequentially so the whole operation of the display could be understood.

We will be arranging an alternative to the "AND" display, should supplies become difficult to obtain. Don't forget you can make your own 7 segment display and have no supply problems.

cont. on p17.

SAVE... with ELLISTRONICS

289 LATROBE ST. MELBOURNE. 3000

Steve Ellis offers:

- *Fast SELF SERVICE
- *Speedy MAIL ORDER
- *14 Staff —all keen
- *2,000 Semiconductors
- *8,000 Components
- *LOW - LOW PRICES

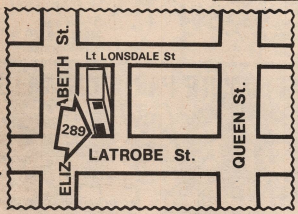

Please use this order form or a photocopy to keep our records NEAT

To:

STEVE ELLIS, ELLISTRONICS,

289 LATROBE ST, MELB., 3000

From:

post code:

Please supply:

1 — BC547 (free) with coupon. P&P $2 min please	Total $	

ELLIS.....S

289 LATROBE ST. MELBOURNE. 3000
PHONE (03) 602-3282. 602-3836.
TELEX AA37758 LSTRON.

A Must! Weller soldering iron

Made in Australia

25 watt Exempt

$12.75

NEW

$5.75 ea

Soldering iron stand. Heavy, durable, comes with sponge ...

New! JIFFY BOXES

PCB's SNAP IN horizontally
Guides for larger boards

VALUE!

(Less 10% for 10)

UB1 $1.69 + 25¢ tax
UB2 $2.56 + 38¢ "
UB3 $1.35 + 21¢ "
UB5 .81¢ + 8¢ "

Rack mounting box

$34.75

Size: Box 42.6(L) x 25(W) x 14(H) cm

TOP QUALITY SUPPLIED IN FLAT PACK EASY TO ASSEMBLE

FITS STANDARD 48.3 CM RACK, 19" $38.41 inc tax

Value!

$5.95

$6.84 incl. tax

Hornspeaker
5" 8 ohm
Ideal for PA use
Weatherproof

DELUXE METAL CABINETS

Beautifully made with aluminum base and 18 gauge covers. Fitted with rubber feet. louvered for ventilation with attractive two-tone finish. These make excellent cabinets for power supplies, switch panels, remote control units and many other applications.

A: 102 × 56 × 83 $2.17 + 33¢ TAX
B: 150 × 61 × 103 $3.39 + 41¢ "
C: 150 × 76 × 134 $3.78 + 57¢ "
D: 184 × 70 × 160 $4.30 + 65¢ "

Save with Ellistronics!

Bulk buy!

16 DRAWER PARTS CABINETS

$10.86
$12.49 inc tax

★ Stackable — raised rings prevent slip
★ Compact — ideal for workshop
★ Clear view drawers — see at a glance what they contain
★ Useful size — each drawer may be divided up into 4 compartments — 1 divider per drawer is provided
★ Strong plastic cabinets size 300 (W) x 180 (H) x 144 (D) (MM)

THERE WILL NEVER BE A CHEAPER TIME TO RE-ORGANIZE YOUR WORKSHOP.

Our lowest prices ever! While stocks last!

( )

FULL SPEC's PRIME IC's

Use this order form for SPEEDY despatch

bankcard welcome here

( ) 2716 450ns Single 5v	5.95	( ) MB 8414 250ns(2114)	21.00
( ) 2732 450ns - - - -	18.50	( ) 65 x 08 1k x 8 CMOS	9.00
( ) 2114 450ns - - - -	2.75		
( ) 2114 300ns - - - -	2.39	FLOPPY DISC CONTROLLERS	
( ) 2708 450ns - - - -	4.50	( ) FD 1771	21.60
( ) 4116 200ns - - - -	2.25	( ) FD 1791	65.00
		( ) FD 1793	65.00
( ) Z80 C.P.U.	8.06		
( ) Z80A C.P.U.	10.81	8 BIT MPU's	
( ) Z80 C.T.C.	6.95	( ) 6802	10.97
( ) Z80A C.T.C.	8.48	( ) 6808	7.60
( ) Z80 P.I.O.	6.95	( ) 6809	46.77
( ) Z80A P.I.O.	9.18	( ) 6821	5.10
( ) Z80 SIO/0	41.43	( ) 6840	7.86
( ) Z80A SIO/0	53.46	( ) 6845	38.94
( ) Z80 SIO/1	41.43	( ) 6847	28.00
( ) Z80A SIO/1	53.46	( ) 6850	15.33
( ) Z80 SIO/2	41.43	( ) 6852	3.87
( ) Z80A SIO/2	53.46		
( ) Z80 SIO/9	41.43		
( ) Z80Z SIO/9	53.46		

( ) Chemical price list

RISTON 3000 COATED FIBREGLASS BOARD

SINGLE SIDED:

( ) 6" x 3"	1.60
( ) 6" x 6"	2.30
( ) 9" x 6"	3.35
( ) 12" x 12"	7.95

DOUBLE SIDED:

( ) 6" x 3"	2.30
( ) 6" x 6"	3.30
( ) 9" x 6"	4.10
( ) 12" x 12"	9.45

ALL PRICES PLUS 15 PERCENT SALES TAX IF APPLICABLE.

Special! $55.95 exempt

WELLER WTCPN SERIES

LOW VOLTAGE, TEMPERATURE CONTROLLED SOLDERING STATION

A transformer powered soldering station, complete with a low voltage, temperature controlled soldering pencil. The special Weller "closed loop" method of controlling maximum tip temperature is employed, thereby protecting temperature sensitive components while the grounded tip protects voltage and current sensitive components. The soldering pencil features a stainless steel heater construction, a non-burning silicon rubber cord and a large selection of iron plated tips in sizes from .8 mm diameter to 6 mm diameter with a choice of tip temperature of 600°F/315°C, 700°F/370°C and 800°F/430°C.

A redesigned transformer case features an impact-resistant noryl for durability and protection against accidental damage, a quick connect/disconnect plug for the soldering iron, extra large wiping sponge, tip tray to store extra tips, plus an improved off-on switch with a long-life neon indicator light, a non-heat sinking soldering pencil holder and a 2 m flexible 3-wire power cord.

The soldering iron is normally provided with a PTA7–1.6 mm screwdriver 700°F/370°C tip.

SPECIFICATIONS

Power Unit ● Power input 240 Volts 50 Hz 60 Watts Int. ● Transformer Output Voltage — 24 Volts (Full Load) ● Power Unit Size — 113mm x 187.3mm x 92mm ● 2 Metres, 3 Wire Power Cord.
Soldering Pencil ● Soldering Pencil Wattage — 48 Watts ● Tip Voltage *To Ground .01 Volts P-P ● Pencil Weight — 50 gram (W/O Cord) ● Recovery Time (From 100°F Drop) W/PTA7 Tip = 11 Sec.

Special low price...

NEW!

SOAR corporation

ME-501A

$69

$79.35 inc TAX

DIGITAL HANDHELD MULTIMETER . . .

Ushers in a dynamic generation of multimeters

SPECIFICATIONS

VOLTS: DC - 200MV-1000V Accuracy - 0.8% AC - 1000V

CURRENT: DCMA - 200u-10A Accuracy 1.2%

RESISTANCE: 2K-2Meg Ohms TRANSISTOR Hfe CHECKER

Build this!

Intersil LCD 3½ DIGIT PANEL METER KITS

BUILD A WORKING DPM IN 1/2 HOUR WITH THESE COMPLETE EVALUATION KITS

Test these new parts for yourself with Intersil's low cost prototyping kits complete with A/D converter and LCD display (ICL7106CPL) and ICL7116CPL (LED) plus all passive materials including PC board. For a functioning panel meter.

ICL7106EV (LCD)

INTERSIL ICL7106 LCD EVALUATION KIT

$29.50 + $4.43 TAX

See the full range at ELLISTRONICS

Prices plus 15 percent sales tax.

TOP QUALITY LOW COST TRANSFORMERS

R-2150-2851
Primary: 240V AC.
Secondary Voltage: 12.6 volts CT.
Secondary Current: 150mA
Termination: Flying leads.

$2.50 10 up $2.10

R-2155
Primary: 240V AC.
Tapped Secondary Voltages: 6.3, 7.5, 8.5, 9.5, 12.6, 15.
Secondary Current: 1 amp.
Termination: Solder lugs on transformer.

$3.90 10 up $3.51

R-6672
Primary: 240V AC.
Tapped Secondary Voltages: 15, 17.5, 20, 24, 27.5, 30.
Secondary Current: 1 amp.
Termination: Solder lugs.

$6.19 10 up $4.95

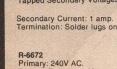

S2000 8" (200mm) wide range general purpose. Includes transformer, mounting holes for P.A. and background use. Very smooth over-all response 45 Hz-12 KHz. Fitted to a 1.3 cubic ft vented enclosure they sound unbelievable.
8 Ohm 8 Watt RMS 5.6 oz magnet.
$6.00 TRADE, $8.95 Inc. tax

EXTRA SPECIAL

2N 3055 TRANSISTORS
FULL SPEC. MOTOROLA
55c ea. plus 15c tax

MJ 2955 TRANSISTORS
65c ea. plus 18c tax

TEXAS INSTRUMENTS CALCULATORS

Ti 25	$19.04
Ti 30 SP	$22.85
Ti 50	$38.09
Ti 55	$54.09
Ti 58C	$141.50
Ti 59	$295.00
PC-100C	$240.00
(Printer/Plotter for Ti 58C and Ti 59)	
Speak and Spell	$77.78
Dataman	$24.26
Little Professor	$17.62
AC9131 AC Adaptor/Charger for Ti 58C/59	$7.06

Calculators plus 15 percent sales tax if applicable. Full range of calculators and accessories in stock.

DIRECT IMPORT PANEL METERS AT LOW, LOW PRICES

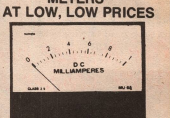

MU-65 1MA — 120 ohms
100uA — 1400 ohms
Dimensions: Overall — 100mm(W) x 82mm(H)
Scale — 100mm(W) x 50mm(H)
Mounting: Hole required — 63mm
Bolts centres — 80mm(W) x 64mm(H)
Nuts and washers provided

$10.18 ea. plus $1.52 tax

MU-45
O-1MA-120 ohms
O-50UA-1400 ohms
O-5ADC-3 Shunt
0-30VDC-100 ohms

$6.45 ea. plus 97c tax

MU-45 VU METER
VU (0dB equals 1mW into 600ohms)
—1,000ohm

$7.35 ea. plus $1.11 tax

MU-45 DIMENSIONS
Overall — 58mm(W) x 52mm(H)
Scale — 56mm(W) x 31mm(H)
Hole required — 44mm
Bolt centres — 38mm(W) x 38mm(H)
Nuts and washers provided
10 or more less 10 percent

Lowest prices ever....

ELLISTRONICS

289 LATROBE ST MELBOURNE 3000
602-3282 602-3836

OVER 10,000 COMPONENT LINES ALWAYS IN STOCK.
CALL IN OR SEND 50c STAMPS (Wait for issue #9!!) FOR FREE FULL-LINE CATALOGUE
SALES TAX CODE B. ADD 15% SALES TAX
A. ADD 27½% SALES TAX

* WHY? WE HAVE JUST TAKEN OVER ANOTHER COMPANY!
* ALL TOP BRAND COMPONENTS- (NATIONAL-FAIRCHILD-MOTOROLA,ETC)
* THERE HAS NEVER BEEN A BETTER TIME TO STOCK UP-BUY NOW AND SAVE A FORTUNE!
* PRICES VALID FOR 2 MONTHS. (OR TILL STOCK RUNS OUT)

Indicate quantity:
eg: (1), (5), (10).
Not: (✓) or (X)

( ) 7400	19¢	B	( ) 74LS38	23¢	B	( ) 74C85	73¢	B	( ) 2N3645	08¢	A
( ) 7410	18¢	B	( ) 74LS40	17¢	B	( ) 74C150	1.08	B	( ) 2N3694	08¢	A
( ) 7420	17¢	B	( ) 74LS42	46¢	B	( ) 74C151	1.00	B	( ) 2N4032	18¢	A
( ) 7430	17¢	B	( ) 74LS47	76¢	B	( ) 74C154	1.52	B	( ) 2N4250	06¢	A
( ) 7432	23¢	B	( ) 74LS51	15¢	B	( ) 74C174	80¢	B	( ) 2N4354	08¢	A
( ) 7440	18¢	B	( ) 74LS74	25¢	B	( ) 74C907	50¢	B	( ) 2N4355	08¢	A
( ) 7441	85¢	B	( ) 74LS86	30¢	B	( ) 80C95	51¢	B	( ) 2N4356	08¢	A
( ) 7442	38¢	B	( ) 74LS90	39¢	B	( ) 80C96	51¢	B	( ) 2N6129	45¢	A
( ) 7447	74¢	B	( ) 74LS109	32¢	B	( ) 80C97	51¢	B	( ) 2N6130	45¢	A
( ) 7448	65¢	B	( ) 74LS112	32¢	B	( ) 80C98	51¢	B	( ) 2N6131	45¢	A
( ) 7450	18¢	B	( ) 74LS113	32¢	B				( ) AY6118	20¢	A
( ) 7454	17¢	B	( ) 74LS114	32¢	B	LINEAR AND MICRO			( ) AY6119	20¢	A
( ) 7490	35¢	B	( ) 74LS122	35¢	B	( ) LM311	47¢	B	( ) AY6121	25¢	A
( ) 7491	48¢	B	( ) 74LS126	47¢	B	( ) LM555	19¢	B	( ) BC547	07¢	A
( ) 74109	34¢	B	( ) 74LS136	34¢	B	( ) LM723	40¢	B	( ) BC548	07¢	A
( ) 74116	1.65	B	( ) 74LS151	42¢	B	( ) LM741	18¢	B	( ) BC549	08¢	A
( ) 74141	75¢	B	( ) 74LS162	60¢	B	( ) 2102	75¢	B	( ) BC557	08¢	A
( ) 74150	56¢	B	( ) 74LS168	$1	B	( ) 2114 300ns	$2.39	B	( ) BC558	08¢	A
( ) 74154	84¢	B	( ) 74LS169	1.07B		( ) 2708 450ns	$4.50	B	( ) BC559	09¢	A
( ) 74173	94¢	B	( ) 74LS173	94¢	B	( ) 2716 450ns	$5.95	B	( ) FT2955	50¢	A
( ) 74181	1.41	B	( ) 74LS174	50¢	B	( ) 2732 450ns	18.50	B	( ) FT3055	50¢	A
( ) 74195	54¢	B	( ) 74LS181	1.70B		( ) 2809	2.50	B	( ) MJE2955	60¢	A
( ) 74196	68¢	B	( ) 74LS196	90¢	B	( ) 4116 200ns	$2.25	B	( ) MJE3055	50¢	A
( ) 74198	1.10	B	( ) 74LS258	97¢	B	( ) MM5740	7.50	B	( ) TIP31A	36¢	A
( ) 74199	1.10	B	( ) 74LS325	86¢	B	( ) 6800	6.95	B	( ) TIP31c	44¢	A
( ) 74365	45¢	B	( ) 74LS353	93¢	B	( ) 6802	$10.97	B	( ) TIP32A	36¢	A
			( ) 74LS365	42¢	B	( ) 6808	7.60	B	( ) TIP32c	47¢	A
74LS SERIES			( ) 74LS368	44¢	B	( ) 6810	3.10	B			
						( ) 6852	3.87	B	DIODES		
( ) 74LS00	18¢	B	CMOS			( ) 8080	2.50	B	( ) 1N914	02¢	B
( ) 74LS02	18¢	B	( ) 4000	20¢	B				( ) BA217	02¢	B
( ) 74LS03	17¢	B	( ) 4001	19¢	B	TRANSISTORS			( ) 1N4001	04¢	B
( ) 74LS09	19¢	B	( ) 4011	19¢	B	( ) 2N2484	25¢	A	( ) 1N5404	15¢	B
( ) 74LS10	16¢	B	( ) 4014	75¢	B	( ) 2N2907	20¢	A	( ) Red 5mm	09¢	B
( ) 74LS11	19¢	B	( ) 4069	18¢	B	( ) MJ2955	63¢	A	( ) Yellow 5mm	9¢	B
( ) 74LS12	16¢	B	( ) 4075	21¢	B	( ) 2N3055	49¢	A	( ) Green 5mm	9¢	B
( ) 74LS13	40¢	B	( ) 4503	51¢	B	( ) 2N3565	09¢	A	( ) Red 3mm	10¢	B
( ) 74LS14	44¢	B	( ) 4511	88¢	B	( ) 2N3567	09¢	A	( ) Yellow 3mm	10¢	B
( ) 74LS15	19¢	B	( ) 4515	$1.70	B	( ) 2N3568	08¢	A	( ) Green 3mm	10¢	B
( ) 74LS21	19¢	B	( ) 4519	33¢	B	( ) 2N3639	07¢	A	( ) Red Rect.	19¢	B
( ) 74LS22	19¢	B	( ) 74C00	18¢	B	( ) 2N3640	08¢	A	( ) Yellow "	25¢	B
( ) 74LS26	23¢	B	( ) 74C02	18¢	B	( ) 2N3641	08¢	A	( ) Green "	25¢	B
( ) 74LS30	16¢	B	( ) 74C04	18¢	B	( ) 2N3643	07¢	A			

cut-off cut-off

OSCILLOSCOPES

Hitachi Oscilloscope V-152 DC-15MHz
Dual Trace ..... $560.00 Ex/Tax $644.00 Inc/Tax
V-302 DC-30MHz
Dual Trace ..... $955.00 Ex/Tax $1062.43 Inc/Tax
V-550 DC-50MHz
Dual Trace ..... $1795.00 Ex/Tax $1996.93 Inc/Tax

Two types of probes extra
AT10AB 1:5:10 to 1 ..... $20.00
Ex/Tax $22.25 ea Inc/Tax
AT10AC 1:5:10 to 1 and 1 to 1 switch $40.00
Ex/Tax $44.50 ea Inc/Tax

SPECIAL OFFER!

Trio Oscilloscope CS-1560A-11, 130mm CR Tube, DC to 15Mhz Dual trace.

ONLY $499.00 EX/TAX

$573.85 INC/TAX

POLY PACK SPECIALS

PP.1 100 Mixed Disc Ceramic capacitors **$1.50**

PP.2 100 Mixed Polyester capacitors Includes values .001uf up to 1uf **$3.00**

PP.3 50 Mixed Electrolytic capacitors, RB. and RT. from 1uf to 4700uf. **$2.50**

PP.4 25 Assorted Potentiometers Includes slide and rotary types. **$2.50**

PP.5 20 Assorted Switches Includes Toggle,Rocker and Slide types **$2.00**

60¢ post and pack. per item

RUSH THESE!!

VERO TYPE BOARD

		Ex Tax	Inc Tax
H5614	90x80mm	$1.17	$1.25
H5602	150x90mm	$2.30	$2.64
H5116	310x100mm	$3.44	$3.96

Plated Strips-Alpha Numeric Grid,the most versatile board of the lot.Etched copper strips are pre-drilled and plated for soldering ease.
These boards have an Alpha Numeric Grid to facilitate positive Pin identification.

PRO-QUALITY 13/.12 TINNED HOOK UP WIRE 8 COLOURS in 100M rolls

BLACK
BROWN
RED
ORANGE
YELLOW
GREEN
BLUE
WHITE

Introductory PRICE

$3.75 ea

Or 8 Rolls for

NEW! **$26.00** EX TAX

29.90 INC TAX

XENON FLASH TUBE

$1.83 ex $210 inc Tax — Trigger Transformer To Suit 60¢

DUAL LIGHT DEPENDENT RESISTORS

60¢ EXEMPT 69¢ INC TAX

REED SWITCH AND COIL

NOW THRASHED TO RIBBONS

SWITCH 34¢ +5¢ Tax
COIL 65¢ +10¢ Tax

DIL PCB SWITCHES

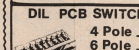

	EXEMPT	INC TAX
4 Pole	$1.00	$1.15
6 Pole	$1.39	$1.60
8 Pole	$1.65	$1.90
10 Pole	$2.86	$3.29

ELISTRONICS WOW!

289 LATROBE ST MELBOURNE 3000
602-3282 602-3836

ALL SUPERB QUALITY PRECISION MADE NEW LAB SERIES

Are You Colour Conscious? You SHOULD BE! Especially when it makes work so easy. "UNISOUND" The Colour Coded multimeters. All Models have battery test too!

DT 1313 20K/Vdc 19 ranges
DT 1314 50K/Vdc 38 ranges
DT 1316 50K/Vdc 36 ranges
& AC AMPS

DT1313 $27.13 $31.19 inc tax

DT1314 $34.54 $39.72 inc tax

DT1316 $35.88 $41.26 inc tax

TUNING GANGS 85¢ ea

ideal MW & SW receivers

WHILE STOCKS LAST!

IC SOCKETS

LOW PROFILE

	TRADE	INC TAX
8 Pin	15¢	18¢
14 Pin	21¢	25¢
16 Pin	24¢	28¢
18 Pin	25¢	29¢
20 Pin	26¢	30¢
22 Pin	28¢	33¢
24 Pin	30¢	35¢
28 Pin	34¢	40¢
40 Pin	52¢	60¢
64 Pin	$1.10	1.27

WIRE WRAP GOLD PLATED 3 LEVEL WRAP

	TRADE	INC TAX
8 Pin	65¢	75¢
14 Pin	89¢	1.02
16 Pin	99¢	1.14
18 Pin	1.02	1.18
20 Pin	1.05	1.21
24 Pin	1.54	1.77
28 Pin	1.65	1.91
40 Pin	1.85	2.13

SOLID STATE REFRIGERATION

601-4000

Low cost experimental service
Minimum ΔT = 30°C
I = 7-8 Amps
V = 3·5 VDE
Hot side Temperature = 50°C
$16.00 plus 15% Sales Tax.

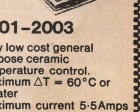

801-2003

New low cost general purpose ceramic temperature control.
Maximum ΔT = 60°C or greater
Maximum current 5·5Amps
Nominal voltage 8 V dc
Hot side temperature 50°C
$32.00 plus 15% Sales Tax.

MAKE YOUR OWN 7-SEGMENT DISPLAY

— Design by Craig Jones

The advantages:

★ Constructed yourself
★ LARGER than available displays
★ Just needs LEDs and PC board
★ Cheap to build

Once again we have designed a SERIES of articles.

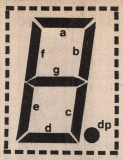

7-SEGMENT DISPLAY

project cost: $6.00

PARTS

1 - "7-Segment Display PC Board"
15 - 3mm Red LEDs

This first part describes a 7-segment display and presents constructional details to build your own. Initially it will be a single digit assembled on a neat printed circuit board. The board has been designed to take up to four digits with multiplexing but that will be something for discussion later.

WHAT IS A 7-SEGMENT DISPLAY?

The names of most electronic items are self-explanatory. This 7-segment display falls into this category. The most common layout for a single digit appears at the top of this article. Each black segment represents a "bar-type" LED which has an overlay of red plastic containing a cut-out design to give the effect of a figure eight. When various combinations of LEDs are illuminated, we obtain the numbers from 0 to 9. The following diagram shows how this is done:

How do you tell if an unmarked display is common cathode or common anode? It's quite simple! You will need 2 penlite cells, a 100ohm resistor and 2 leads with alligator clips. Begin by attaching the negative lead to any pin on the display. Touch each other pin with the 100 ohm resistor. You may or may not find one segment lights up. Keep progressing along the display with the negative clip until you find a position where every segment lights up in turn as the resistor touches the pins. This test shows you have a common cathode display. After all, the circuit you are using is similar to the lower display circuit on the back page DATA shet.

If no segments light, try reversing the leads. When all the segments light, you have a common anode display.

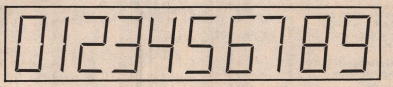

Each segment is given a letter to facilitate easy identification, especially when troubleshooting. The decimal point is represented by "dp" and is handy for decimals or as a seconds dot. Segments b,c represent 1, segments a,b,d,e,g, represent 2, through to "0" being represented by a,b,c,d,e,f.

Some driver IC's provide a top to the number six and a tail to the number nine, as shown in the diagram. The output of other IC's exclude this feature. It depends entirely on the driving network built into the chip and cannot be altered.

7-SEGMENT DISPLAY: COPPER SIDE

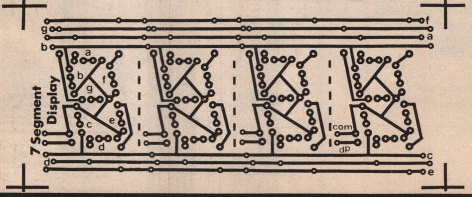

7-Segment Display

Light Emitting Diode displays are made in two basic styles. Common cathode and common anode. With the first type the cathode of each LED is connected together to form a common line. To create a common anode display, merely reverse each LED. Our display will replace any available unit, it just depends on the orientation of the LEDs. Here is a list it will replace:

COMMON CATHODE DISPLAY:

FND 357
FND 367
FND 500
FND 800
DL 704
DL 750
MAN 1A
MAN 10A
MAN 4740A
MAN 6750
MAN 74A
Z-4103

COMMON ANODE DISPLAY:

FND 350
FND 360
HP 5082 7620
" 7630
" 7640
" 7650
" 7660
" 7670
DL 707
DL 727
DL 747
MAN 52A
MAN 53A
MAN 72A
MAN 73A
MAN 82A
MAN 4710A
MAN 6730
Z-4117

A side benefit of the 7-Segment layout is its ability to form letters of the alphabet. Use the space below to see how many letters you can create using the standard layout at the beginning of this article. Try producing both upper and lower case letters. You will be surprised how many can be formed:

By itself, the display isn't much fun. You need to connect it to a driver IC to get any effective results such as numbers or letters. The driver is a set of transistors which turn on the display segments in groups to produce the numbers 0 - 9. These transistors receives their "turn-on" information in binary form in which the signals will be as HIGHs and LOWs. To create the numbers 0 - 9 from say a push button we need to pass through a number of stages. It is not possible to merely count the number of times a button is pressed to display the number on the module. The various encoding and decoding stages will be discussed in the next section. They are quite involved but extremely interesting. The circuit we will be presenting will contain separate IC's for each stage. Unlike the counter, which contains all the sections within the one chip,this series is designed to teach you in stages.

CONSTRUCTING AND TESTING

The PC board is designed as a 4-digit module. It can be cut between the digits to produce a single or multi- digit display and is designed for multiplexing. This series uses a single digit with 15 LEDs and it is suggested that the balance of the board be left attached for later extensions. Connect the 15 LEDs as shown in the diagram to produce the common cathode display. Keep the soldering neat and snip the leads at the solder line. The digit can be tested as discussed earlier with 2 penlite cells and 100 ohm dropper resistor. You will notice pairs of LEDs are connected in series to give the effect of a rectangular LED. Ideally this display needs a transparent red perspex cover-plate and should be viewed from a distance since the digits are fairly large. It is designed to be seen across a room and will be useful for such projects as clocks and lap counters.

Build the display now!
Wait for the next issue....

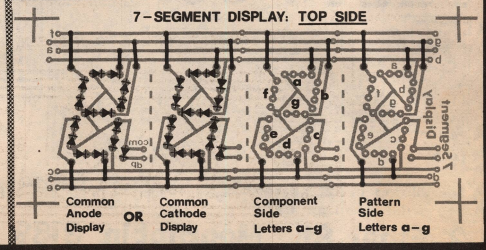

AUST.-WIDE ELECTRONIC SUPPLIERS:

Be carefull This is a list of manufacturers and parts suppliers. They don't all sell small parts for experimenters. Some just make one particular electronic part such as a zippy box, PC boards or books. If in doubt, ask first or use a supplier nearest to you or known by his past performance.

A.C.E. Electronics, 136 Victoria Rd., Marrickville, 2204 51 3845
ACME Engineering Co., 2-18 Canterbury Rd., Kilsyth, 3137
Adaptive Electronics, 410 St Kilda Rd., Melbourne, 3004 267 6800
Advanced Electronic Systems, 3/33 Glenhuntly Rd., Elsternwick 3185 523 9098
AIWA Australia, 14 Gertrude St., Arncliffe, 2205
A.G.S.Electronics., 7 Orchard Rd., Brookvale, 2100
All Electronic Components, 118 Lonsdale Rd., Melbourne, 3000 662 3506
Altronics, 105 Sterling St., Perth, 6000 328 1599
Antex Electronics, Box 285, Chatswood, 2067
Applied Technology, 109 Hunter St., Hornsby, 2077 487 2711
Atkins Carlyle, 44 Belmont Ave., Belmont, Perth, 6104
B.P.Electronics, 11 Duke St., Albany, 6330(098) 41 2681
B.J.D. Electronics, 202 Bourke St., Melbourne, 3000
L.E.Chapman, 122 Pitt Rd., North Curl Curl, 2099 (02) 93 1848
Circuit Components, 383 Forrest Rd., Bexley, 2207 59 3720
CQ Electronics, 30 Campbell St., Blacktown, 2148 621 5809
Cristie Hand, Box 48 Epping, 2121
Ray Cross Electronics, 151 Boronia Rd., Boronia, 3155 762 2422
Datson, 29 Dukes Crt., Phillip, 2606
Dandy Electronic Discounts, 508 Bridge Rd., Richmond, 3121 428 6887
Delsound, 1 Wickham Tce., Brisbane, 4000 229 6155
Direct Disposals, Box 165, Fortitude Valley, Brisbane, 4006
D R Hi-Fi, 657 Pittwater Rd., Dee Why, 2099 (02)982 7500
David East Components, 33A Regent St., Kogorah, 2217 588 5172
Diggerman Electronics, Box 33, Cooranbong, 2265(066) 54 4212
Eastern Communications, 898 Riversdale Rd., Camberwell 3124 836 0635
Bill Edge's Electronic Angelfish, 115 Parramatta Rd., Concord 2137 745 3077
Electronic Distributors, Shop 4 90 Arcade, Joyce St,PendleHill 2145 636 6566
EMONA Enterprises, Box 188 Coogee, 2034 212 4815
Electronic Development Sales, 32 Chandos St., ST. Leonards, 2065 438 2500
Electro Voice, 174 Taren Point Rd., Taren Point, 2229
Elltinstrics, 289 LaTrobe St., Melbourne, 3000 602 3282
ELMEASCO instruments, 21 Anthony Dr., Mt. Waverley, 3149
Entronics, 640 George St., Sydney, 2000 211 0531
Experimenter Parts Co., 2 Ethel St., Moorabbin, 3189 557 4182
GB Telespares, 504 Queensberry St., N. Melbourne, 3051 328 4301
G.C.S. 67 Blacksmith Ave., Mordiale, 2223
Hi-Q Aerials, 69 Maitland Rd., Islington, 2296 61 5317
Hunts Electronics, Box 546, Toowoomba, 4350
In - Electronics, 84 Railway St., Chatswood, 2067
IMARK, 167 Roden St., W. Melbourne, 3003 329 5433
International Correspondence Schools, 18 Collins St, Melb 3000
Jatronics, Box 31 Engadine, 2233
Jaycar 380 Sussex St., Haymarket, Sydney, 2000 264 6688
Jensen Electronics, 75 Prospect Rd., Prospect, 5082 (08)269 4744
J.R. Components, Box 128, Eastwood, 2122 (02) 85 3976
J.R. Components, 123A Bathurst St., Hobart, 7000
Kit-Sets, 293 St. Pauls Tce, Fortitude Valley, 4006
K. Tronics, 260 Wright St., Adelaide, 5000
Linear Electronics, Box 254, Punchbowl, 2196

Lookey Video, 418 Bridge Rd., Richmond, 3121 (03)429 5674
Mc Gills Newsagency, 187 Elizabeth St., Melb 3000
Magrath & Co., 208 Lt. Lonsdale st., Melbourne, 3000 663 3731
Marconi School of Wireless, Box 807 Archbardt, 2040
Melbourne Printed Circuits, 6 Bulli St., Moorabbin, 3189 553 1744
Microtics, Box 175, Randwick, 2031
Mode Electronics, Box 365, Mascot, 2020
Modular Computer Systems, Box 103, Round Corner, 2158
Morganic Industries, Box 127 Oakleigh, 3166 543 5166
Mostyn Enterprises, Box 134, Rydalmere, 2116
N.E.T. 38 President Ave., Caringbah, 2229 525 6090
Orbit Electronics, Box 7176, Auckland, New Zealand.
Plessey Components, Box 2, Villawood, 2163
Pow-Pak Electronics, 1a West St., Lewisham, 2132 569 9770
Radcon Quality Components, 105 Eldridge St., Bankstown, 2200 709 4706
Radio Despatch Service, 869 George St., Sydney, 2000 211 0816
Radio House, 760 George St., Sydney, 2000
Radio Parts, 562 Spencer St., W. Melbourne, 3003 329 7888
RCS Radio, 651 Forest Rd., Bexley, 2207 587 3491
R&C Electronics, Box 68, O'Halloran Hill, 5158
David Reid Electronics, 127 York St., Sydney, 2000
David Reid Electronics, 356 Lonsdale St., Melbourne, 3000 602 4673
Rifa Pty Ltd, 202 Bell St., Preston, 3072 480 1211
Rod Irving Electronics, 425 High St., Northcote, 3070 489 8131
Rogers Electronics, 44 Heather Dr., Para Vista, 5096
Scope Laboratories, 3 Walton Ave., Airport W. 3042 338 1566
Semiconductor Imports, Box 43, Croydon, 3136
Semikron Electronic Components, 239F Glenvale Cres, Mulgrave, 3170 561 3476
Senis, 2 Guildford Lane, Melbourne, (Mail order only) 3000
Sheridans Electronics, 95 Regent St., Redfern, 2016 699 6912
Michael Sheridans Electronics, 164 Redfern St., Redfern 2016 699 5922
Silicon Valley, Box 898, Crows Nest, 2065
Silicon Valley, 22 Ross St., Newstead, 4006
Dick Smith Electronics, Box 321, North Ryde, 2113 888 3200
Soanar Electronics, 30 Lexton Rd., Box Hill, 3128 89 0661
Stewart Electronics, 44 Stafford St., Huntingdale, 3166 543 3733
Stotts Technical Correspondence College, 159 Flinders Lane, Melb. 3000
Talking Electronics, 35 Rosewarne Ave., Cheltenham, 3192 550 2386
Tandy Corporation, Box 229, Rydalmere, 2116
Tasman Electronics, 72 Victoria St., Launceston, 7250 354 5062
Technical Book & Magazine Co., 295 Swanston St., Melbourne, 3000
Tehnitron, 63 Grange St., Bundaberg, 4670 72 5606
Television Replacements, Rear 139 Union Rd., Surry Hills, 2137 89 1019
United Trade Sales, 317 Swanston St., Melbourne, 3000 663 3815
Vernon Engineering, PO Box 130, Paddington, 2021
VICOM, 339 Pacific Highway, Crows Nest, 2065
VICOM, 68 Eastern Rd., Melbourne, 3000 699 6700
W F Heathkit Centre, 228 Park St., S. Melbourne, 3205
Wireless Institute of Australia, 14 Aichieson St., Crows Nest, 2065
Zenith Electronics, 6 Bank St., Box Hill, 3128 88 6825

Specializing in all parts used in TALKING ELECTRONICS projects
See order form on P27

2 Ethel St., Moorabbin 3189

everyone can learn electronics . . . the effective Heathkit® way!

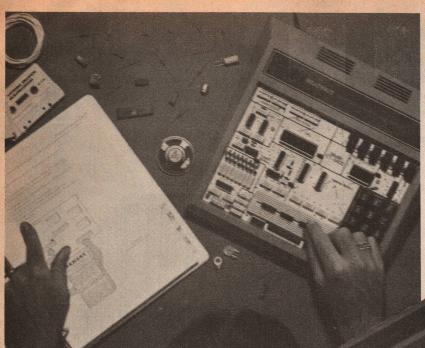

There's never been a better, faster, lower cost way to learn electronics than these Heathkit Programs! Learning electronics could very well be the most important step you'll ever take, so, naturally, there are many factors to consider in choosing your method of learning. If you're like most people, you don't have the time for conventional learning institutions. The Heathkit Continuing Education Series was conceived to make learning electronics more convenient and affordable for everyone. Thousands of people just like you are finding out what makes Heathkit learning programs so tremendously successful. Simple, easy-to-use and EFFECTIVE!

Among the many reasons for the wide acceptance of these programs is their simplicity. Each learning program is simply and logically arranged for easy, step-by-step 'programmed' learning. Progressing at your own established pace, you learn in an unhurried environment free from pressure. No facet of the material is omitted and nothing is assumed. Each program includes everything you need for a high degree of understanding. Audio records (or optional cassettes) reinforce the text material and an optional final examination lets you test your overall comprehension.

The Continuing Education Programs are economical too. The first four programs use the same trainer so you can get a complete education in fundamental electronics at substantial savings. The advanced programs, Digital Techniques and Microprocessors, require separate trainers, but they still cost less than competitive courses.

Get 'Hands-on' experience for a better understanding of electronics. Learning electronics and being able to apply what you've learned are, of course, the goals you seek to achieve with the Heathkit Continuing Education Series. For that reason, we have spared no effort in assuring your complete comprehension. Our optional Electronic Trainers, designed for use with each program, perfectly illustrate the Heath approach to learning. These trainers give you actual 'hands-on' experience with electronic components and circuitry. It's an acknowledged fact that you learn best by doing and the trainers let you do exactly that. You get a better grasp of circuit concepts and perform the program projects quicker and easier as well. Solderless connectors on the trainer panel make hookup of the components supplied with the program quick and neat. Built-in power supplies and signal sources provide convenient operation. The trainers are available in both kit and assembled form.

When you've finished the program, the trainer still serves as the ideal device for breadboarding circuits of your own design. We highly recommend these trainers as supplements to the Heathkit Individual Learning Programs. A record (or cassette) player is needed to play the audio portion of the material. A VOM for measuring voltages is also needed, and an oscilloscope is required for some of the experiments in the Electronic Circuits and Digital Techniques Programs.

to find out more send for your FREE CATALOG today!

Recommended Order

The Heathkit Self-Instruction Programs are Designed to let you Progress from DC Electronics to AC Electronics to Semiconductor Devices to Electronic Circuits. These are the Four Basic Programs. For Optional Advanced Study, The Digital Techniques Program Provides the Background for the Microprocessor Program.

There are many courses in the HEATHKIT Continuing Education Program designed to effectively expand your electronic horizons including:—

EE3101	DC Electronics	$84.00
EE3102	AC Electronics	$92.00
EE3103	Semiconductors	$92.00
EE3104	Electronic Circuits	$109.00
EE3201	Digital Techniques	$134.00
EE3401	Microprocessor Program	$168.00
ET3100	Experimenter/Trainer	$149.00
ET3200	Electronic Trainer	$166.00
ET3400	Computer Trainer	$415.00

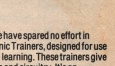

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for $..... is enclosed plus $7.00 for package and post.

Name .....

Address ..... **P/Code** .....

Send to: W. F. Heathkit Centre
220 Park St., South Melb. 3205. Phone 699 4999.

☐ EE3101
☐ EE3102
☐ EE3103
☐ EE3104
☐ EE3201
☐ EE3401
☐ ET3100
☐ ET3200
☐ ET3400

☐ Please rush me my Free catalog containing full details on the complete range of Heathkit Learning Programs.

Bankcard Credit Card No:

Expiry Date _____ Signature _____

WF15 1180

PRE-CUT P.C. BOARDS

Two new 10-board packs.
Pre-cut to fit jiffy and zippy boxes!

SINGLE SIDED KIT — $3.50

DOUBLE SIDED KIT — $4.50

P&P $2

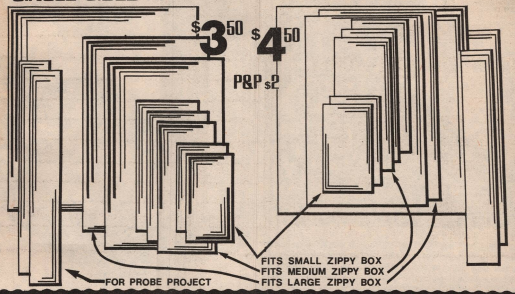

HELP!! It doesn't work!

Don't forget, all the projects in the magazine are guaranteed to work. If they don't; don't despair! Try a little friendly persuasion on the circuit, check and double check everything. Ask a friend...get a little technical advice. If all this fails, try sending it to the man who designed it. Try sending it back to the magazine. For $3 we will look over your effort and try to get it going. If it is made on one of our PC boards, it will have a lot more hope. To avail yourself of this service, send the unit in a jiffy post bag size '00' with $3 plus $1 for any parts it may require, together with your name and address and a few words about the fault. Incl 80c in stamps for return postage. We like these little teasers as they help us up-date our projects for the next issue.

Vero battery box

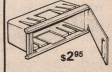

$2.95

VEROBOX large 6.80
" med. 4.20
" small 1.95

vero / veroSTRIP

VERO STRIP — $2.00 ea.

$1.85

$3.25

No. 60 Drill: 85c

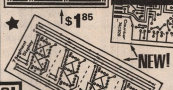

NEW!

$3.95

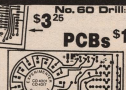

PCBs $1.80

$3.75

20 Transistors $2.40!

As used in 'THE TRANSISTOR PAGE' experiments...
ALL NEW! ALL GUARANTEED! HURRY!

TYPICAL TYPES: BC 547, 548 BC 557, 558 etc.

All boards fibre glass

TV service transistors!

BU 126 - $1.20
BU 208 - $2.80

TALKING ELECTRONICS mag,

35 Rosewarne Ave., Cheltenham 3192.

Post & Pack:
1 board 60c
others 25c ea.

95c

PRE-PAK
14 WEST ST., LEWISHAM, 2049
P.O. BOX 43, CROYDON, 2132

Name_____

Address_____

Postcode_____

ORDER FORM

Circle your item. Write your order. Total $

MOLEX PINS

Both the 74C926 and the AND 4145 display are mounted on molex pins. We have found this to be a fairly successful form of mounting as the 24 pin display has different in-line width to a normal 24 pin IC socket. Molex pins also allow you to remove both chips for other projects as most of the cost is centered in these items. The 4-digit 7 segment display described in the next article is fully compatible with this project and the AND display can be substituted with your own home-made version.

MOUNTING THE PARTS

Commence assembly by fitting the molex pins. Cut them into lengths of the exact number of pins required. Push into place and solder quickly and neatly. Bend the unwanted runner backwards and it will break off from the pins. Fit the 4 transistors, 5 jumpers and battery leads. Finally solder all the resistors, including the 7 dropper resistors chosen from the enclosed list.

Now comes the two expensive parts. Locate the dot on one corner of the 74C926. Do not go by the lettering or numbering on the IC. It is not always printed around the same way. Only go by the tiny dimple or dot or key-way in one end. The AND display has a locating mark as a notch or recess in its lower side. Refer to the drawing. With these in position, it is ready for testing.

TESTING

Connect a lead with an alligator clip to the positive rail. This will be your test lead. Connect the battery or power supply and the display will illuminate with 0000. Tap the alligator clip onto the resistor marked "clock" and the display will register 1 or maybe 5 or 6 depending on the number of spikes it detected. You can reset the counter by touching the resistor marked "reset".

Next issue we will provide some experiments and details on input sensors.

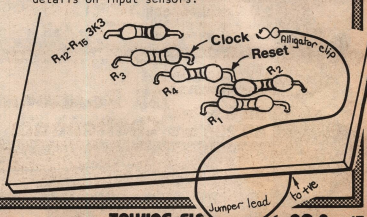

PRE-PAK

Name_____

Address_____

Postcode_____

ORDER FORM

Circle your item. Write your order. Total	$

PARTS BY THE Kgm!!

We have loads of NEW miniature components ideal for electronic projects

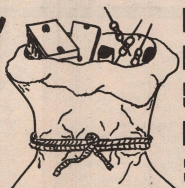

EDSALL PARTS
Factory 2
53 Keys Rd
Moorabbin
3189

553 1824

$25 Value!

250gm bag of mixed components for $4

Plus $1 p&p

Typical assortment: 50 ¼w & ½w resistors, 20 capacitors, trim pots, mounting parts, transistors, 10 electrolytics, diodes, slide switches, knobs, pots and clips.

WHICH BOX?

A time will come when you will want to house your projects in a neat enclosure. Maybe because you are proud of your efforts or embarrased by the messy construction. Either way you will want to protect the circuit from general handling and abuse. A huge range of enclosures is available to protect your masterpiece and it would be extremely handy to have a visual comparison for cross-reference. The diagram below does just this. It compares three major manufacturers size:size. Before deciding on the most suitable size, check the pro's and con's of each style:

Battery Compartment:

Convert any box to a box with battery compartment with the Vero battery holder. Merely make a cut-out 58mm x 24mm and press-fit the compartment into the box. It has 4 fingers to automatically grip the inside of the box. You may like to seal it in position with silicone sealant. The lid is self-hinged and snaps closed. The price is high but the finish is really good.

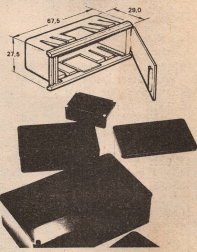

ZIPPY & JIFFY UB2 H 2752 $3.75

VERO LARGE $6.80

ZIPPY & JIFFY UB1 H2751 $2.50

ZIPPY & JIFFY UB3 H2753 $1.95

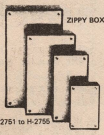

ZIPPY & JIFFY UB4 H2755 $1.50

VERO SMALL $1.95

VERO MEDIUM $4.20

EXACT BOX SIZES

MAKER:	DICK SMITH	"ZIPPY" / "JIFFY" ALTRONICS	VERO
QUALITY OF FINISH	VERY GOOD	VERY GOOD	EXCELLENT
LID TYPE	ALUMINIUM	ALUMINIUM	PLASTIC
FITTINGS	4 PHILIPS	4 PHILIPS	4 PHILIPS SCREWS
MOUNTING & SITTING	Can be mounted or sat on any side or top or bottom		
LID FITTING	Aluminium lid sits within wall thickness on 4 studs. The studs can be removed only with great difficulty.		Plastic cover fits over the top of the box with 4 screws. Studs can be removed at base with little difficulty.
MOUNTING PARTS ON SIDE OF BOX:	All sides are fully ribbed and increases the effective thickness to double. Difficult to mount pots and switches. Use lid or base.	Only a few ribs on each long side. Easy to mount parts. PC boards also sit horizontally on ledge 10mm from bottom.	No ribs at all. You will need to make your own fitting arrangements, via a glued block. Don't drill and spoil the box.
PRICE:	Both similarly priced.		40% more expensive. Finish is 50% better.

.....Continuing the

EXPERIME

LED DICE

...WITH SLOW DOU

PROJECT SIX

Each project in this series needs just a few extra components in addition to the previous project to create a completely different circuit and add a new dimension to the possibilities of electronics. This is one such circuit.

Being electronically minded, have you ever wished you could throw away the old dice used in snakes and ladders and replace it with an electronic dice? Well now you can. With this LED DICE the full realism of waiting for a dice to stop rolling or a spinner to stop spinning is re-created with an electronic circuit. It works like this: after placing your finger on the TOUCH PLATE the LEDs begin to flash rapidly. After a second or two they reduce speed to a running sequence. Then they slow down to a walk and finally a crawl. At this stage you are hoping they will jump one more step to make a six. You're in luck! It jumps to a six! But wait, the capacitor may not be fully discharged. You will have to wait a few more seconds to see if the 555 oscillator will clock the CD 4017 one more step. It does. You lose. You get a single solitary ONE for your turn.

That's the luck of the game. I've never been lucky at cards, dice or poker but I'm sure this game will bring you luck. Even if you don't win at Ludo or Monopoly you will generate a lot of interest from your family and friends - especially since there is no way of "loading" the circuit; it gives a completely random unbiased result.

How it works:

When the battery is connected, the BC 557 transistor Q_1 is biased off via resistor R_2. This means that no voltage will be present at the collector. When the TOUCH PLATE is touched with your finger, C_1 charges and provides a base-emitter potential to turn on Q_1. This potential must be higher than the turn-on voltage of .6v, to turn on Q_1. The collector now provides a voltage at its output. Pin 7 of the 555 timer detects this voltage as described in the beginning of the series. It will oscillate at a frequency determined by the voltage on pin 7 and the value of C_2.

When your finger is removed from the TOUCH PLATE the voltage on capacitor C_1 is gradually removed via the two 10M bleed resistors. As this voltage reduces, the base voltage reduces and the transistor provides a reducing voltage at its collector and also on pin 7 of the 555 oscillator. Thus the output frequency of the 555 slows down and finally comes to a complete halt.

The output of the 555 drives a CD 4017 decade counter which lights each LED in turn. We are using 6 of its 10 outputs. So that only the first six are clocked, the 7th output is connected to the reset pin number 15.

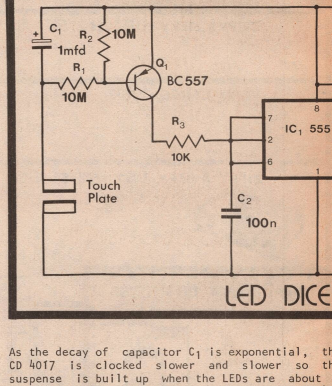

As the decay of capacitor C_1 is exponential, th CD 4017 is clocked slower and slower so th suspense is built up when the LEDs are about stop. You will never quite know whether the CD 40 will clock just one more time or sit on your luc number six!

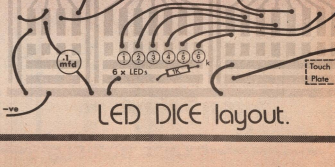

DOWN IN THE DUMPS AND LOOKING FOR A BARGAIN ?

.... Don't miss out on these

MONEY SAVERS

PRE-PAK ELECTRONICS

COMPARE THE VALUE!

"Wow! Look at these fabulous Bargains!"

HURRY! LIMITED STOCKS

C90 High quality low noise fully g'teed tapes at bargain price!

Best quality compact cassette

BUY 10+ $1.10ea.

$1.35 EACH

RECORD CLEANER ARM $2.99

Cassette Tapes AMPEX C-90 HIGH QUALITY $1.99 EACH EXTRA LOW NOISE!

MAGNETIC CARTRIDGE $9.99 DIAMOND

STEREO HEADPHONES

VOLUME AND TONE CONTROLS FOR EACH CHANNEL

$9.99

$29 LCD ALARM

SALE PRICE!

DIGITAL WATCHES quartz

MENS ALARM WATCHES, DAY, DATE, HRS, MINS, SECS

ALL WATCHES GUARANTEED FOR 6 MONTHS.

LOW COST LCD WATCHES HOURS, MINS, SECS, DATE, BACK LIGHT. Ideal Xmas Gift! LADIES

MENS OR LADIES $14.99

ALL ARE AVAILABLE IN GOLD OR STAINLESS STEEL FINISHES

MENS

BOYS OR GIRLS $12.99

UNISEX WATCH $19

LADIES FASHION WATCH $19

We give you quality and after-sales service, too.

Not illustrate CHILD'S MICKEY MOUSE WATCH only $10

PRE-PAK ELECTRONICS PTY. LTD

NEW LOW PRICES

LOOK Phone orders 24 hours a day

1a WEST ST LEWISHAM

N.S.W. PH: 569-9797

PACK/POST: ADD 10% ORDER VALUE

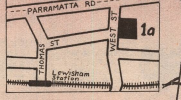

FASTER MAIL ORDER SERVICE

open 7 days

MON-FRI : 9:00AM - 5:30PM
SATURDAY : 9:00AM - 5:00PM
SUNDAY : 10:00AM - 4:00PM

bankcard welcome here

MAIL ORDER PACK AND POST - PLEASE ADD 10% TO COVER COSTS.

P.O. Box 43, CROYDON. 2132

DON'T DELAY!

electronics of the future.

COMPARE THE VALUE! PRE-PAK ELECTRONICS

NEW CLIP-IN PUSH BUTTON PHONE DIALLERS

Instal in mins! Only 5 wires to connect!

$29.99 Now SAVE $10 (RRP $39.99)

Specially designed to replace Aust. rotary dials. Not approved by Telecom under current reg.

Loudspeaker Phones

We have several loudspeaking phones available -

BASIC MODEL $95

WITH PUSH-BUTTON DIALLER $119

DE-LUXE MODEL WITH HANDSET ALSO $169

SUPER DE-LUXE WITH 50 MEMORIES $395

2, 3, 4 STATION INTERCOM

MASTER/SLAVE combinations, 9v batt. or AC adaptor ($8.50), up to 150 metre range, easy to instal, all wiring supplied, all guaranteed.

2 STATION - 1 master, 1 slave, was $14.50, now $12.50

2 STATION - Doorphone, was $16.90, save $3. now $13.90

3 STATION - 1 master, 2 slave, was $25.90, now $22.50

4 STATION - 1 master, 3 slave, was $37.50, now $28.50

TELEPHONE INTERCOM ALL MASTER SYSTEM

$39 For private and also simultaneous conversations, new wall or desk mounting models are easy to instal- 6 mths g'te 2STATION - 9v batt. $39 PR 2STATION - DOORPHONE SET with 'open' button, $41.50 PR 2-10 STATION ALL MASTER - supply 12v dc ¼A ($11.50),3 wire plus extra 1 for each station used, easy to instal with instructions supplied.$29.90 EA.

KAMBROOK solid-state FM Wireless INTERCOM

Use anywhere in the house or office, only $45 each

We have a large range of intercom communication systems for home, office or factory. We'll supply the equipment for you to do-it-yourself, or we can arrange installation.

AUTO DIALER TELEPHONES

Using Dialer as above!

DESK MODEL $75.00

WALL MODEL $69.95 (not illustrated)

NOT APPROVED BY TELECOM

RINGING WITH FEATURES

NEW DE-LUXE MODEL WITH 99 NUMBER MEMORY $229

RCA MicroComputer

$149

FULL DETAILS

VP-111

SEND FOR SALE

Assembled and Tested
Easy to Program and Operate
1K Static RAM — Expandable to 32K
512 Byte ROM Operating System
Video Interface
Audio Cassette Storage Interface
On-Board Tone Generator
Fully Expandable

Just add power and make connections to your video monitor or rf modulator and home TV and you're ready to go. Simple instructions allow you to start programming immediately.

On board interface allows you to add on colour displays, music, system prototyping, control functions and other applications.

Includes 1K memory, you can add an extra 3K on board. Input is through an integral 16 key hexidecimal keypad.

An audio cassette recorder enables memory contents to be saved and reloaded for long term date storage - interface provided.

Built-in audio tone generator can be used for verification of user commands.

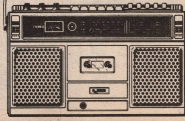

$17 MM/FM Quartz Traveller Clock Radio. Full IC circuit, wake to music or buzzer. DC IUM3x4 radio, UM3x1 clock). 185 x 80 x 45mm.

NEW CLOCK-RADIOS

- the latest features
- the very best quality

$22 AM RADIO LCD CLOCK BUZZER ALARM

LED clocks

$15.99 MAINS OPERATED BRIGHT LED DISP LOUD ALARM

calculators

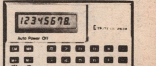

$12.99 A most practical LCD calculator 4-keys memory with % & √. SUPER-THIN POCKET-SIZE AUTO-OFF

CASSETTE RECORDER BATTERY/MAINS

Piano type Cassette Tape Recorder, built-in condenser microphone, auto stop and ALC DIN jack.

$34 De-Luxe model go anywhere portable - at a low, low price!

FM SW MW LW STEREO RADIO CASS-RECORDER

DE-LUXE PORTABLE WITH HI-FI SOUND - 4 BANDS RADIO WITH STEREO CASSETTE RECORDER - FEATURES TAPE COUNTER, INBUILT MICROPHONES, PUSH-BUTTON CONTROLS, ONLY A LIMITED QUANTITY AVAILABLE AT THIS SPECIAL PRICE!

$119

ALL REDUCED!

PRE-PAK ELECTRONICS

COMPARE THE VALUE!

WHOLESALE PRICES

DIGITAL LED CAR CLOCKS

•12v Thin-line auto Quartz –70x45x20c
•Self-adhesive back sticks to car dash!
•Automatic night dimmer

$16.99

12v DIGITAL CAR CLOCKS
• ALARM • GREEN DISPLAY
• AM/PM • ABOVE/BELOW DASH

•QUARTZ CRYSTAL ACCUR.
•AUTOMATIC NIGHT DIMMER
•24 HR. ALARM SYSTEM
•REV. POLARITY PROTECT.

$24

BATTERY CHARGER WITH METER 4½" x 3½" x 2½"

SAVE $3

$29.90

12v 4-AMP

ALSO TRICKLE-CHARGER 12v 0.5amp WITHOUT METER $11.50

RED FLASHING LED

car alarm

Entry (8 seconds), Exit (30 seconds) time delay, alarm reset after 2mins, instant alarm to protect accessories etc, relay outlet to flash parking lights or car horn etc. REDUCED $10 TO...

$59

LEDLUX

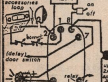

A theft warning system for vehicles by coded radio signal....

$109

AUTO-PAGE transmitter alerts your personal pager up to ½ mile distance. Two microphone sensors attached to car body triggers alarm before actual entry occurs. Ideal for motor bikes, 4 wheel drive vehicles, trucks, caravans, etc.

UNIVERSAL CABLE KIT $1.95

Interchangeable pins, colour coded leads, with instructions

PANEL SOCKET 90c

LESON

Hand-held compression mic with big CB/Amateur talk-power.

WAS $22.50 now $15.50 SAVE $7

ANTENNA BOOSTER

Wide band RF amp improves AM/FM radio reception like you wouldn't believe! GTEED

$9.99

Highway Hi-Fi

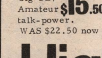

$39

Auto-Stop Fast Forward 4W Output

STEREO CASSETTE PLAYER

AM/FM Car Stereo.

AUTO REVERSE CASSETTE AM-FM STEREO RADIO-IN-DASH

$139

AM/FM STEREO RADIO CASSETTE

AUTO-STOP CASSETTE FAST FORWARD LOCAL-DX SWITCH IN-DASH MOUNTING.

$79

AM CAR RADIO $19.99

FAMOUS MAKER WITH SPEAKER - IN-DASH INSTALLATION

GRAPHIC EQUALIZER 20w+20w BOOSTER

$59 for Car Hi-Fi Systems Includes 5 stage graphic equalizer with LED bar-graph VU display. Includes fader control, outputs 4-ohms.

was $69 SAVE $10

CAR STEREO BOOSTER

30W + 30W 4 OHMS BIG SOUND! EASY INSTAL.

$34

Car stereo speakers that think they're home stereo speakers.

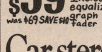

5¼" SPEAKERS with BIG SOUND PERFORMANCE

PR $39

COAXIAL SUPERIORITY

3-WAY SPEAKER SYSTEM

$69 PR.

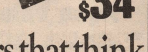

COMPLETE IN BOX READY TO INSTAL.

FERRIS, Air suspended 3 Way Speaker System, 5 inch 10 oz. Magnet Woofer, 3 inch Midrange, 1 inch Horn, 40 Watts Max.

50W

PR $79

SOUND-BARRIER 9"x6" 50 watt 3 way Co-Axial speakers are about THE BEST. We have other similar speakers as low as $55, but these really handle heavy rock. A woofer, mid-range and tweeter, in one great combination!

SOUND-BARRIER 5" twin-cone super-thin 20W 8ohm speakers

PR. $26

COMPARE THE VALUE! PRE-PAK ELECTRONICS

SAVE MONEY..

*NEW BIG POWER Speaker Systems

ETI 4000/2 KITS 150 W RMS

JUNE ETI 3 WAY

SPEAKERS and X'OVERS $360 PR.

INCLUDING CABINETS $498 PR.

Kits are all complete with screws, wire, Velcro tape and crimper networks are sound, ready to install. Cabinets are assembled and ready to fit speakers.

do-it-yourself

3-13L PLAYMASTER SPEAKER KITS 80w $175

E.A. DEC '79

SPEAKERS $115 PR BOXES ONLY $75 PR

ETI 4000/1 KITS

156w RMS

FEBRUARY ETI 4 WAY

SPEAKERS and X'OVERS $460 PR.

INCLUDING CABINETS $698 PR.

PHILIPS

25w 8Ω 3 WAY SPEAKER KIT SALE!

WALNUT Finish, ready-made boxes, black speaker cloth.

8 WOOFER+5 MID-RANGE+ 3 TWEETER + X'OVERS + wire and Inner bond + screws!

SALE

•Can be finished in 2 hours!
•Great sound!
•.55Hz-18KHz resp.

KITS PER PAIR $69

OR ASSEMBLED & TESTED PR $109

Super Values!

2½" (57mm) Philips tweeters, 8 ohm 20W rating only.....$3
4" (100mm) Novik mid-range, 8 ohm 20W rating, only.....$5
5" (127mm) Rola mid-range/ tweeter, 8-15 ohms 15W.....$3
6½" (165mm) Magnavox twin-cone speaker, 8 ohms 7W.....$6
8" (200mm) Imported woofer, 8 ohms 20W rating.....$8

HI-FI SPEAKERS

12"	30W twin driver, 20-3000Hz	ea	$29.90
10"	25W twin driver, 34-6,000Hz	ea	$19.75
8"	20W twin driver, 40-6,000Hz	ea	$11.90
8"	20W dual cone, 40-16,000Hz	ea	$12.95
5¼"	30W mid-range, 800-6,000Hz	ea	$ 6.95
4"	25W mid-range, 800-6,000Hz	ea	$ 4.50
1"	25W dome tweeter, 400-20,000Hz	ea	$ 6.95
1"	50W dome tweeter, T 20 kHz	ea	$11.00
3"	25W cone tweeter, T 20 kHz	ea	$ 5.50

LAST AT 80 PRICES

CROSSOVERS

2 Way 30W FIMS, 5 kHz, 6dB/Oct	ea	$ 3.95
3 Way 40W FIMS, 1 kHz, 6 dB	ea	$ 6.95
3 Way 50W FIMS, 600 Hz, 3 kHz, 12 dB	ea	$12.50

CORAL SYSTEMS DO-IT-YOURSELF

CORAL AUDIO

High quality, famous name kits, complete with speakers, crossovers, mtg. screws, terminals, name badges, instructions for building cabinets to suit and installation. — 8 ohms

6SA 1	6" 2 way 30W, 50Hz-20kHz pair	$ 88	SAVE
8SA 1	8" 3 way 35W, 70Hz-20kHz pair	$ 99	
8SA 5A	8" 2 way 35W, 50Hz-20kHz pair	$ 99	
10SA 1	10" 3 way 50W, 40Hz-20kHz pair	$129	
10SA 5A	10" 3 way 50W, 40Hz-25kHz pair	$169	
12SA 1	12" 3 way 60W, 30Hz-20kHz pair	$189	

SAVE HEAPS

TURNTABLES

BSR Belt-Drive TURNABLE $105 Sent Freight On

NEW MODEL
• FEW ONLY!
• FULLY AUTOMATIC OPERATION

With base, cover and ADC mag. cart!

ECONOMY TURNTABLE $79 Freight On

BSR Semi-Auto rim drive with base, cover and cartridge

Available about June, 2 new straight-arm turntables, complete with base, cover and quality mag. cart. The semi-auto belt-drive will be around $119 while the direct-drive model will sell at around $179. Write for more details soon!

NEW DOLBY DECK

CASSETTE $139 DECK (Sent Freight On)

EXPO Front loading model with DOLBY

• TWIN VUS
• BIAS SWITCH
• EQUAL. SWITCH
• TAPE COUNTER
• GUARANTEED 1 YEAR GOOD
• SOUNDS GOOD

8 OHM TWEETERS

New High Quality Ultra-wide dispersion, 2-20KHz, 102 dB 1m/1w, for even low power speakers, 50w rating 9.50 ea.

Were $14.50 Save $5

NEW HIGH QUALITY GUARANTEED X'OVER NETWORKS

2 WAY	30W	5KHz, 6dB 2.90
3 WAY	40W	1KHz, 6dB 6.25
3 WAY	50W	600Hz, 12dB 8.50
3 WAY	80W	3.5KHz, 12dB 12.90

Hz, 12dB

New 'HORNY' SPEAKERS

FOR SIRENS, ALARMS or PA.

3½" 5W Metal $8.25
5x4" 8W Plastic $10.50

8"x4" ALL 8 OHMS

HEAVY DUTY MODELS

6" 15W All Metal $21.50
8" W " $25.75
8"x5" W " $25.75
12" 25W " $38.50

SUPER SAVER!..

$7 8Ω 7W 5" HORN SPEAKER!

SPEAKER VOLUME CONTROLS
Constant impedance "L" pad for 8ohms, 15w rating $5.50
100 watt rating.....$7.95
Fitting instructions incl.

WALL MOUNTING CONTROLS
5w for background music etc. Also has sockets for 1 or 2 speakers, "L" pad, 8ohms
Mono $7.95, Stereo $11.50
Screw terminals for easy connections, fits std. electrical wall fittings.

SPEAKER ATTENUATORS
8ohm 18 watts RMS level controls for MID-range or HIGH-range
Attenuation 0.5 to 30dB
MID or HIGH.....14.50ea

SPEAKER TERMINALS
Red and Black on panel.....$1.20
As above on black aluminium recessed cup 100mm diameter.....$1.95

SPEAKER CROSSOVER CAPACITORS
Non-polarised, 50V, pigtail leads,

1uF	.35¢	4.7uF	.50¢
2uF	.40¢	8uF	.55¢
3uF	.45¢		

JUNIOR PUZZLE PAGE

How do you begin to learn electronics? By playing and experimenting! This page is for beginners. These simple puzzles will start you learning and thinking. Try them.....

1. The border around this page is made from a chain of diodes. There is one odd-man-out, Can you spot it?

Do you look but don't see? What can you see in this diagram? Turn it around.

3. A square field made from four resistors encloses one diode. How many diodes will eight resistors enclose?

4.

5.

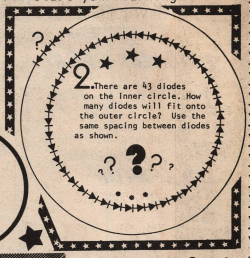

2. There are 43 diodes on the inner circle. How many diodes will fit onto the outer circle? Use the same spacing between diodes as shown.

OUT

Help Granny Diode out of the Capacitor Maze. Start in the middle and work your way out.

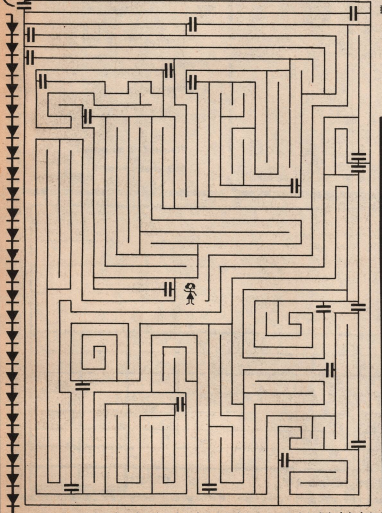

6. I have a zippy box and wish to cover it with a piece of clear perspex. The only piece I have has 4 holes in it as shown. How can I obtain a perfectly clean piece of perspex 80mm x 50mm from this damaged sheet?

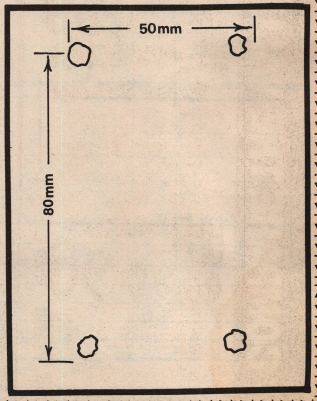

TALKING ELECTRONICS
A New Magazine for Experimenters

COUNTER MODULE

( ) 7 - 100R ¼ 3k3
7 - 180R ¼ 1M
7 - 220R ¼ BC 547
7 - 180R
7 - 100R
1 - 74C926 IC
1 - AND 4145 display
Enclose $15.50 plus $1 P&P.

7 SEGMENT DISPLAY

FOR ONE DIGIT:
( ) 15 - 3mm Red LEDs
enclose $1.50 plus 60c P&P.

FOR FOUR DIGITS:
( ) 60 - 3mm Red LEDs
enclose $6.00 plus 60c P&P.

LED ZEPPELIN

( ) PARTS LIST:
1 - 270R ¼w
1 - 330R "
1 - 390R "
3 - 470R "
1 - 560R "
3 - 1k "
2 - 2k2 "
1 - 3k3 "
1 - 4k7 "
1 - 10k "
1 - 22k "
1 - 56k "
1 - 470k "

1 - 4.7mfd 16v
1 - 470mfd 16v
7 - BC 547
1 - BC 557

1 - CD 4001 IC

6 - Large red LEDs
1 - Mini red LED

2 - 1N 4148
1 - Push-on switch
1 - battery clip
Enclose $5 plus $1 P&P.

TALKING ELECTRONICS
A New Magazine for Experimenters

LIGHT THE LED

PARTS LIST:
( ) 2 - 22k ¼w
2 - 2k2 "
1 - 1k "

1 - BC 547

1 - 4.7mfd 10v

6 - 1N 4148

1 - Red 5mm LED

1 - CD 4017 IC

1 - Battery clip

1 - Springy brass strip

Enclose $3.00 plus 60c P&P.

EXPERIMENTER BOARD

( ) PARTS LIST:
For circuits 1-5

1 - 1k ¼w
1 - 2k2 "
1 - 10k "
1 - 100k "

1 - .01mfd ceramic
1 - .1mfd ceramic
1 - 10mfd electro 10v

1 - 555 IC
1 - CD 4017 IC

1 - PE cell ORP12
or similar
2 - Red LEDs
1 - Push-on switch
1 - battery clip
Enclose $5.30 plus $1 P&P.

( ) Circuit 6:
2 - 10M ¼w
1 - 1mfd 16v
1 - BC 557
6 - 5mm Red LEDs
30cm hook-up wire

Enclose $1.05 plus 60c P&P.

TALKING ELECTRONICS
A New Magazine for Experimenters

EXPERIMENTER DECK

( ) Projects 1 - 10

1 - CD 4001 IC
1 - CD 4017 IC

1 - 15R ¼w
1 - 22R "
1 - 120R "
1 - 3k3 "
2 - 4k7 "
5 - 10k "
1 - 47k "
1 - 100k "

1 - 1n 100v
1 - 3n3 "
1 - 3n9 "
3 - 6n8 "
2 - 22n "

1 - 4.7mfd 10v
1 - 22mfd 10v

6 - 1N 4148 diodes

1 - 100k cermet VTP
1 - 500k " "

24 - Red 5mm LEDs
1 - Green 5mm LED

1 - BC 557
3 - BC 547

1 - 2½" spkr 8 or 15Ω

30cm of 10-core ribbon
30cm tinned copper wire
Roll of fine solder

Enclose $11.50 plus $1 P&P.

Name: .....

Address: .....

.....

Please find enclosed
MO/cheque for $_____

TO .....

.....

.....

FROM .....

.....

.....

PLEASE SUPPLY:

(P&P 10% OF ORDER) **TOTAL $**

FREE!

We bought 20,000 perfect, A1, unused BC 547 and BC 557 transistors. We are offering them at the trickle-rate of 2 per customer.

Yes, I know it's only small, but it's a start! To keep costs low, I suggest you combine with a couple of friends. Just include a stamped addressed envelope. You can get one BC 547 now or wait for the next issue for you BC 557.

Please send a free BC 547 transistor to:

NAME _____

ADDRESS _____

_____

Don't forget the stamped addressed envelope.

RULES:

- No need to buy anything.
- Offer valid for 6 months.
- No stamp needed when including an order.
- Must include coupon.
- No photocopies!
- You can combine with your friends in the one envelope.

Subscription

$7 FOR ISSUES 3-8

( ) I enclose cheque/M.O. for $7.00

Name_____

Address_____ Post Code_____

PC BOARDS: (✓)

NEW! Now you can get your PC boards JUST PRINTED, ready for you to etch yourself. Save time yet have the satisfaction of completing it yourself.

( )	Counter Module with 42 Molex pins	3.25
( )	Four Digit Display	3.95
( )	Light the LED, just printed	60c
( )	" " " finished	95c
( )	LED Zeppelin, just printed	1.00
( )	" " undrilled	1.50
( )	" " drilled	1.80
( )	Experimenter Board 3-ICs printed	1.10
( )	" " " finished	1.85
( )	Exptmr Deck, 10 pins printed	2.50
( )	" " " " undrilled	3.40
( )	" " " " drilled	3.75

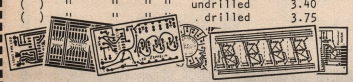

( )	"VEROBOARD" 100mm x 150mm 34 track	2.00
( )	"10 PC board kit" 1 sided	3.50*
( )	" " " 2 sided	4.50*
( )	PC board BLANKS 200mm x 200mm	2.00*
( )	" " " 200mm x 400mm	3.50*
( )	10 PC board " " "	30.00*
( )	No 60 drill	85c
( )	PC kit to make your own boards	7.00*
	*post and pack:	2.00
( )	Pkt of 20 transistors	2.40
( )	100 transistors: 50 BC547,50 BC557	9.00
( )	8 pin IC socket	20¢
( )	14 pin IC socket	25¢
( )	16 pin IC socket	30¢

Name_____ Please find enclosed MO/cheque for $_____

Address_____ Post Code_____

Post & pack 1st item: 60¢
each additional " 25¢

TALKING ELECTRONICS Magazine,
35 Rosewarne Ave., Cheltenham, 3192.

SHOP TALK

— CONDUCTED BY THE EDITOR

Starting a magazine is like starting a whole new career. The effort required to start such a venture is enormous. There are so many separate departments to organize. Writing, typing, drawing, layouts, printing, distribution, advertising, accounting, etc. etc. Most of these are now settled. We are beginning to get some feedback from shop sales and mail order sales. Together with letters, calls and discussions it looks like being a real winner. Parts sales and magazine sales have been very encouraging and have fortunately been above the estimates of two consulting firms. So many letters of appreciation have said the same thing, viz:the need for a magazine containing constructional projects for beginners with a back-up supply of readily available parts. Some have backed this by ordering every item on the ORDER FORM page! I think that speaks for itself. Talking about speaking for itself. The magazine will only talk if you show it to a friend. I know it's a great danger lending the magazine. More often than not it's never returned. To overcome this I have a plan for the third issue. Many readers value the magazine so greatly that they do not want to cut out the order forms..they make a photocopy! A promotional venture will be conducted in issue three. We will include a copy of issue No 1 in the centre for you to give to a friend. I know you will choose wisely who you will give the magazine to as the introduction will gain you a friend for life. If only I had a magazine such as this when I was venturing into electronics...I would be 10 times more advanced now!

CORRECTIONS TO VOL1 NO1

Page 6: The output sequence in column 3 line 3 should read 3-2-4-7-10-1-5-6-9-11. The diagram is correct.
P 19: Experimenter Deck Parts List should include 24 Red LEDs and 1 green LED. The total kit price becomes $11.50.
P 34: The link below pin 1 of CD 4017 should be higher as shown in issue 2. Actually it is not used until project 2. The diagram in issue 2 has been corrected.

The LED ZEPPELIN circuit on P11 shows incorrect gates for a CD 4001. It should show 3 NOR gates. Change it NOW! Also on P11, under HOW THE CIRCUIT WORKS, we said the circuit consists of a three-inverter CMOS oscillator. Even though the NOR gates are wired as inverters we should be more specific and say: WIRED AS A RING OF THREE CMOS CLOCK OSCILLATOR. In addition, the PC board has pins 11, 12 and 13 left unconnected. As with all CMOS devices, all unused gates should have their inputs connected to ground or V_{SS}. This means pins 12 and 13 should be connected to pin 14.

LETTERS

From our assortment of mail this month we received an interesting letter from Mr. T. Baitch. He is concerned about our choice of symbols for resistors, diodes and crossing points for conductors. He suggest we should use the symbols as stipulated by the SAA. This would mean a typical circuit such as the TICKING BOMB would alter to:

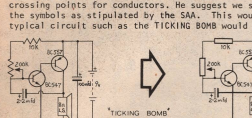

Which circuit do you prefer? Which has more life...more character. After all, the circuits in the magazine are its most important feature. They should instantly present a mental picture of the function of the circuit....without weighing you down with symbol interpretation. I know I was brought up on zig-zag resistors and jumpers for non-connected wires and I feel there can be no mistaking their function. Since most of the symbol-changes have been introduced to simplify circuit drawing and not to improve them technically, I am not prepared to accept them for this reason alone. To me a symbol must give an instantaneous impression of its function. I think the old symbols do this perfectly. Your ideas on this would be welcome. I hope to get a cross-section from old and new readers so we can analyse the results.

ARTICLES

Our reference to a career and submission of articles for publication received an encouraging response. The range and suitability of projects was in line with our format, namely simple digital designs. However they all required a degree of rewrite and sprucing up before final presentation. Accordingly I have formulated a short list of rules for writers:

1. Don't write run on sentences not using commas as they are hard to read.
2. On the other hand, don't use commas, which aren't necessary.
3. Its important to use apostrophe's correctly.
4. Verbs always has to agree with their subjects.
5. Don't use the word "then".
6. Try to not ever split infinitives.
7. Proofread you copy carefully to see if you any words out.
8. When using hyphens at the end of sentences always hyphenate at syllables.
9. Correct speling is essential allways.

OK then lets get to work and see what projects you can come up with for the magazine as we like to see new ideas coming into the establishment and you will receive a small reward for your efforts as described in last issue providing your article is good enough that is.

ANSWERS TO JUNIOR PUZZLE PAGE

1. The bottom right-hand corner contains the reverse-biased diode. 2 marks.
2. CIRCLE OF DIODES: If you guessed the answer, no marks. If you measured the number of times the set of four diodes would fit around the outer circle...3 marks. If you worked out the ratio of the diameters of the inner and outer circles you would know the diodes would be in the same ratio. 4 marks If you drew a line from the ends of the outer 4 diodes to the centre of the circle and found the ratio to be 4 diodes to 3 diodes you would conclude that the outer circle would contain 4/3 x 43 or 57 diodes 6 marks.
3. 4 diodes would be enclosed by 8 resistors. 2 marks
4. Finding your way out of the maze: 2 marks
5. If you see one black and one white man looking up and one black and one white looking down, give yourself 4 marks. You should be able to see the same when the circle is turned around. This indicates you have 2 different depths of focus and is vital.
6. If you bought a zippy box and placed it on the sheet, give yourself 4 marks. If you tried with pen and ruler or mathematics. Give yourself 2 marks. In this world we need more practical people and less theorists.

HOW DO YOU RATE?

As an experimenter you will be required to actually participate in producing each month. It is not sufficient to get a vicarious pleasure from the magazine. You need to apply yourself. See how you score from last month: At the end of the magazine is a simple quiz. If you filled it out last month, give yourself 10 points.
Applying yourself is an important part to learning. Saying "I'll leave it till tomorrow" doesn't benefit you at all. Just reading doesn't help either. To a practical person, like yourself, reading only gets you 10% of the way. Constructing adds a further 30% while another 60% is added when a fault develops during construction and you are required to "trouble-shoot" the project and locate the fault.
If you constructed a project from last issue (or even 2 or 3 projects) give yourself 20 points.
If you sent away or purchased additional components, give yourself 10 points.

How did you score? Add up the marks or points and give yourself a rating out of 60.

LOW, LOW PRICES.

DISCO EQUIPMENT

Recommended by Studios for Home, Group & Semi-pro use

$92

- 2 Hi-Lo microphone inputs
- 2 Magnetic/Ceramic phono inputs
- aux tape and tuner inputs
- 2 VU meters ● Stereo or mono
- Independent CUE on each chan.
- Compact size, 16x26x6 cms.
- 9v Battery operation, EXT. DC input socket.

NEW MIKE MIXER Same specs as above, EXCEPT 4 MIKE INPUTS with master control **$64**

the PRO model
WITH 5 BAND GRAPHIC EQUALIZER
Now Only

$179 was $199 Save $20
STEREO
MIXER WITH EQUALISER

- Facilities for 4 stereo program input and 2 mic. inputs
- Built in low noise preamplifier for magnetic phono and low or high impedance microphones
- Professional stereo slide controls
- Headphone controls to monitor each input and output
- Talk switch to reduce stereo volume 14dB so mic's can be used without readjusting music level.
- 5 channel stereo graphic equaliser section using separate slider controls
- Meters monitor the output of left and right channels independently.

CANNON PLUGS & SOCKETS

LOOK! 'SPECIAL' PRICES!
XLP-3-11 PLUG **3.20**
XLP-3-32 SOCKET **2.**
XLP-3-31 SOCKET **3.95***
XLP-3-12 PLUG **.0**
COMPATIBLE
240v AC PLUG XLP-LNE-11 **$4.66**
240v AC PANEL SOCKET XLP-LNE-3212-9A **$5.00**
240v AC LINE SOCKET XLP-LNE-1214-3A **$6.00**

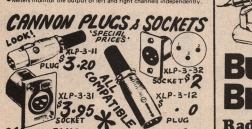

SAVE $3
240v LIGHT FLASHERS
Complete, wired with lamp holder (no globe) HANDLES 60W GLOBE, UP TO 300W WITH H'SINK
Ideal for blinking Advertising signs, Discos etc. was $5.95
$2.95

LIGHT DIMMER KITS OR MOTOR SPEED CONTROL

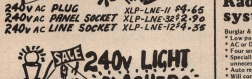

700 watt capability WITH RFI SUPRESSION
$4.95 OR 2 FOR $9.00

PROFESSIONAL MICROPHONES

NEW, ECONOMY FM WIRELESS MIKE $14
Range to 300ft, use FM Radio, size 103x34 x23mm

FM WIRELESS MIKE NEW! $23.90 ea
88-106MHz ELECTRET CONDENSER
ONLY

FM "SNEAKY" SUPER-MICRO TRANSMITTER
Not toys, but highly sophisticated, sensitive 'BUGS'
USE YOUR FM RADIO TO RECEIVE

- X-8 88-93 MHz 800m $74.50 N/W
- X-18 88-108 MHz 3,000m $121.50 N/W

Useing the latest condenser microphone, mercury cells and transistors for small size (X-8 12x35x9mm, X-18 29x55x20mm)

- DT-8 88-92 MHz 300m $92.50
  DT-8 IS TELEPHONE TRANSMITTER 'BUG'
  No batteries-powered from phone line
- MT-3 88-108 MHz 250m $49.50
  MT-3 is an induction pickup phone bug! Place below or behind phone - also, can tell you when phone rings IF in backyard.

General purpose DYNAMIC, with stand etc ← 100Hz-10KHz, 50K imp, was $19.50, save $6, now only... **$13.50**

General purpose ELECTRET CONDENSER 50Hz-13KHz 600 ohms imp, was $22.50, save $6, now... **$16.49**

Burglar Alarm Breakthrough

Radar-Sensing security systems

$249

Burglar & Fire Alarm System.
* Low power consumption.
* AC or DC transfer.
* Four sensing monitors.
* Specially designed exit and entrance delay circuit to avoid unnecessary triggering of alarm.
* Auto reset circuit.
* Will connect with automatic lighting, intercom, amplifier etc.
* For home, office, school etc.

THE SILENT SENTINEL MICROWAVE
Ideal for large rooms and office, shop and factory areas. Range: 18 metres max. Coverage: 90 deg. horizontal. Supply: 12V DC at 170mA, wall mounting, adjustable angle of coverage, adjustable sensitivity. NO or NC contacts.
$159

NESS CONTROL MODULE.....$49.50
Adjustable entry/exit, NO and NC instant and delayed alarm, adjustable reset time, variable siren pitch, bell output, vibration sensor analyzer etc.

KEYSWITCH PLUS 2 KEYS.....$6.95
PRESSURE MAT-use under rugs, mats, etc...$14.95
INERTIA SWITCH-for glass, gates, fences..$17.50
We have LOTS more alarm parts, incl. metal foil tape, terminals, magnetic reed switches, coiled cables, rechargeable batteries and power supplies etc.

METAL CONTROL BOX WIRED.....$49.50
Fitted with key-switch, tamper-switch, LED etc.
Ready for control module and horn speakers.
ELECTRONIC SIREN MODULE.....$14.50
Suits up to 2 horns, adjustable pitch.
ELECTRONIC SIREN SPEAKER.....$17.95
Bi-built circuitry for wailing siren, 12V oper.
ADJUSTABLE TIMER MODULE.....$28.75
1 to 30 mins, with or without auto reset.
OUTDOOR HORN SPEAKER BOXES.....$14.90
White or brown, with tamper-switch.
7W BOHN HORN SPEAKERS.....$7.50

PRE-PAK ELECTRONICS

COMPARE THE VALUE!

JUST LOOK AT THIS

COMPARE THE VALUE! PRE-PAK ELECTRONICS

JUNIOR WALKIE-TALKIES

PER PAIR, NOW ONLY—

$16.99

1 Watt 2 Channel TRANSCEIVERS

- ADJUSTABLE SQUELCH CONTROL
- AUTOMATIC GAIN CONTROL
- SIGNAL-CALL-SYSTEM

Famous maker, with RF stage, two xtals, 27-280 X-tals fitted aircraft incl.

$45 ea

C.B. SENSATIONALS

AM CB MOBILE

SCOOP BUY of these great Vector American 23 channel CB radios at this ridiculous price.

We also have available a good selection of 18 and 40 channel sets –

Apollo 18ch AM	$115
Craig 40ch AM	$105
Fanon-Courier 18ch AM	$89
As above, digital display	$99
Apollo 18 ch AM/SSB	$245
AM 18ch AM/SSB	$225
President 18ch AM/SSB	$229
Super Jaguar 18ch AM/SSB	$219

LOTS MORE – TRADE-INS ACCEPTED!

CB LOCK MOUNT FOR UNDER-DASH SAFE MOUNTING USUALLY $9.95

$7.99 each

5W EXTENSION SPEAKER FOR DASH MOUNTING ETC. FULLY ADJUSTABLE, 8 OHMS USUALLY $10.50

$8.99

$5.99 TVI FILTER

POWER SUPPLY **$39**

Type no: ECA140
Input: 220 to 260 volts 50Hz
Output: 13.8 volts D.C. at 2 AMPS
Ripple: 0.76 mV/Volt at 2 AMPS
Knee Current: 2.5 AMPS
Short Circuit Current: 0.8 AMPS
Load and Line Regulation: 1%

IGNITION NOISE KIT

Prevents interference reaching your CB. 12V only.

$2

MULTI-PURPOSE BASE

For mirror or roof-rack mounting Available with American 3/8" or Scalar base.

$7

HEAVY DUTY BASE

American 3/8" base for 6' to 9' whip aerials

$7.99

QUICK-RELEASE ADAPTOR

Just push and lift! For Scalar or American 3/8" bases.

$5.99

DE-LUXE GUTTER-GRIP

Fully adjustable to suit all cars etc. For Scalar or American

$6

STANDARD SCALAR BASE

Suits all Australian-made aerials

$3

UHF COLLINEAR BASE STATION AERIAL $46.50

Easy to install omni-directional aerial with extremely high performance. Gives 6.5dB gain for boosted signal power.

A ROYCE MARINE ANTENNA.....$29.95
Suits fiberglass or timber boats – no ground-plane.
B WHITE F'GLASS MARINE ANT.$29.95
Suits all boats, caravans, etc. – no ground-plane.
C ADJUSTABLE HELICAL ANT...$24.95
Available in 5' or 3'6" sizes, Scalar base.
D ROOF OR BOOT-LID MOUNT...$10.95
Popular base-loaded antenna, easy to install.
E DE-LUXE GUTTER GRIP ANT..$18.95
With foldover clip – saves damage in low garages and carports.
F DE-LUXE MAGNETIC MOUNT...$15.95
Powerful magnet won't damage duco, use to 80 M.P.H.
G AM/FM/CB LOCK-DOWN ANT...$24.95
Won't be damaged or stolen – recesses below guard.

12v CAR CASSETTE TAPE HEAD DEMAG. PROBE

RESTORES OUTPUT AND H.F. RESPONSE

$1.99

SCOOP! Save $5 were $6.99

ELECTRONIC CASS. HEAD DEMAGNETIZER

R.R.P $19.95
Save $3.95
$16

*RESTORES LOST OUTPUT LEVEL AND RESPONSE *USES HF TRANSISTORIZED OSCILLATOR & MERCURY COIL *GUARANTEED RESULTS *SAFE-TO-USE!

5 Pin DIN → 5 Pin DIN LEAD $2.25 1.3M LONG ea

 

HOBBY IRON 12v 1.5A SPECIAL **$3.50**

GE Ni Cad Batteries

and Chargers now in stock at economical prices. Included are Penlight, C, D cells and 9v PP3 batteries.

The first price is batteries only, the second includes charging module.

Penlight cells, pack of 2	$0.49	$10.39
C size, medium, pack of 2	$0.99	$10.89
D size, large, pack of 2	$9.49	$11.29
PP3 9V, small individually	$10.99	$11.89

Mains powered charger to suit charging module.....$8.05

BATTERIES FOR ELECTRONIC APPLICATIONS AND DIGITAL WATCHES

S – silver-oxide C – carbon zinc
A – alkaline M – mercury

343	M1.35v	$1.95	505	C22.5v	$4.80
354	M1.35v	$1.95	576	S1.5v	$1.65
384	S1.5v	$1.95	EPX13	M1.35v	$2.85
386	S1.5v	$2.25	EPX675	M1.35	$2.85
389	S1.5v	$2.25	E91	A1.5v	$0.75
391	S1.5v	$1.35	E92BP2	A1.5v	PR32.20
392	S1.5v	$1.95	E132	M2.8v	$5.90
393	S1.5v	$2.25	E133M	M4.2v	$7.20
395	S1.5v	$1.95	E134M	M5.4v	$8.35
412	C22.5v	$2.10	E625	M1.4v	$2.75
504	C15v	$3.60	E640	M1.4v	$4.15

CRASH GO PRICES!

6·5MHz CRO
130mm 5" TUBE

$259 DELIVERED FREE! Australia Wide

* WITH INTERNAL CALIBRATION * SHIELDED CO-AX INPUT * FOCUS, INTENSITY AND HORIZONTAL GAIN CONTROLS * ALL SOLID STATE OPER.

Specifications:
VERTICAL DEFLECTION —
HORIZONTAL DEFLECTION —
SENSITIVITY: 50Z MV/DIV
TIME BASE —
SWEEP RANGE: 10 Hz — 100 KHz
SYNCHRONIZING —
Internal and external

TOP TRADE-INS TOO

Much better than similar 3" 75MHz models-see for yourself!

NOW AVAILABLE EX STOCK *

EZ SCAN AC VOLTAGE DETECTOR PROBE

$39 HAND HELD, BATTERY OPER. Place near electric circuits over 60V up to 6.6Kv will light depending on voltage. Indicates live or neutral, up to 150m range. Use to check broken wires, tar ignition leads, faulty appliances, hidden electrical cables etc. or any AC field. SAE for brochures.

SUPER VALUE
* Power Transformers

Input- 200 to 250v in 10v steps. Output- 110v NOW ONLY $19

2A Cont. rating 4A Intermittent.

BUY NOW WHILE STOCK LASTS!

SAVE OVER $4. SOLAR PANEL WITH REFLECTORS R.R.P. $24-50 $19.90

DC: 3v, 6v, 9v 50mA out at full sunshine

Size 104 x 144 x 13mm without reflectors!

Elect Aust June '79 DIGITAL ELECTRONIC LOCK KIT!

WITH PUSH-BUTTON KEYBOARD

$15

Ideal, inter-acting for all beginners, enormous range of possible combinations, all quality parts with full instructions supplied.

TRANSFORMERS

All new, 240v input, guaranteed by Mail

No.		
85	0-6V-18v 1A	4·50
811	26v 1A, 6·3v 1A	4·50
761	31v 1A, 6·3v 1A	4·90
101	50v 1A x 2 windings, 6·3v	5·50
110	110v ·3A, 16v 1A	5·90
112	200v C.T. ·1A, 6·3v 5A	6·00
185	12v ·5A, 26v 1A	3·95

5 METRES ONLY! 5m Speaker Cables 50¢ COLOUR-CODED TOO!

Speakers

6"x2" 5Ω	4" 15Ω	5" 35Ω	5"x4" 15Ω	6"x2" 15Ω
$1.90	$1.50	$2	$1.50	$1.95
5" round 4 or 8Ω	6" round 4 or 8Ω	6¾" ell 4 or 8Ω	7"x5" ell 4 or 8Ω	9"x6" ell 4 or 8Ω
$5	$6	$5.90	$6	$7.25

A — RIPPER — OFFER

SAVE ON ZIPPY BOXES

	Plastic/Aluminium lids	Price
UB-1	150 x 90 x 50mm ea	$ 1.85
UB-2	196 x 113 x 60mm ea	$ 2.95
UB-3	250 x 160 x 90mm ea	$ 4.75
UB-4	300 x 200 x 90mm ea	$ 5.95

BUY 10 - SAVE 20%

The economical way To house all your small projects.

EHT TRANS.

NT3100 NT3101 NT3122 All 3 New ONLY $4.50 EA

3 POS 10A ROTARY SWITCH

HEAVY DUTY

COMPLETE WITH POINTER KNOB Single pole 48V mounting ⅜" hole $0.50¢ EA

220v AC RELAYS

4 pole Plug-in 10 Amp Contacts SOCKET $1 ea $2.65

Cheap Power Switching!

CERAMIC CAPACITORS

POPULAR REPLACEMENT

Look! STEREO $2.50 ea or 3 for $10

BUY-BUY-BUY 25 for $5

MINI DIL SWITCHES

PROFESSIONAL QUALITY, SPACE SAVING, LOW PROFILE. FOR IC SOCKET OR PCB MTG.

8 PIN 4 WAY $2 | 14 PIN 7 WAY $3 | 16 PIN 8 WAY $3.50

NEW!!

35 WAY 2-SIDED EDGE CONNECTOR 0·1 PITCH

WE HAVE A LIMITED QUANTITY OF PYE 0.1 INCH PITCH PCB EDGE CONNECTORS WITH 70 GOLD-PLATED CONTACTS AT ABOUT HALF USUAL PRICE. BE QUICK BUY 10+ $3.90 ea. 100+ $3.50 ea.

$4.50 EA.

100,000uF 16VW COMPUTER QUALITY ELECTROS 10+ New Siemens $9 EA

WERE $12 ea

Miniature 1000hm Trimpots

EA $10

LOOK

PL-259 PLUGS PUSH-ON with In-built reducer! 10 for $5·50 40¢

ELECTRICAL TERMINAL

10+ 40¢ BLOCKS 50¢ SET OF 12

FANTASTIC BARGAINS!

100 ¼W resistor assortment	0.75
100 ¼W resistor assortment	$1.00
200 ¼W resistor assortment	$2.00
250 ¼, ½, 1W resistor asst	$2.00
500 ¼W resistor assortment	$2.00
50 ½, 1% precision resistors	$2.00
100 asst. ceramic capacitors	$2.00
50 asst. mica 2, 5% hi-stab caps	$2.00
30 various Greencaps	$2.00
6 asst. ferrite rods, aerials	$2.00
6 asst. tuning gangs PVC mini	$2.00
12 metres asst hook-up wire Scals	$1.00
20 asst. potentiometers	$2.00
25 asst preset pots	$2.00
30 3,5,7,10 watt resistors	$2.00
40 radio/TV knobs	$2.00
50 assorted tagstrips	$2.00
45 assorted electrolytics	$2.00
20 HF/IF/OSC coils assorted	$2.00
20 assorted VDR's + instr.	$2.00
12 asst. switches, slider, etc.	$2.00
12 fuses asst. 500mA to 20A	$1.00
15 tubular caps, 5 x 5 values	$2.00
12 asst trimmer capacitors	$2.00
30 asst chokes, RF, video, etc.	$2.00
10 built-in cereat trimpots	$1.00
10 12V 120mA globes, wire leads	$1.00
12 pot-nuts and washers	$1.00
8 6.3V MES dial lamps	$1.00
10 MC-2 neons, 90V oper	$1.00
10 metres spkr cable, col-coded	$1.00

TUNING GANGS FROM ONLY EA. $1.95

2 GANG, MSP, 200pf, 90pf. $1.95

3 GANG, MSP, 200/90/200. $2.95

MAGNETIC Cartridges FROM ONLY

$11

Deluxe Jelco magnetic cartridge for popular replacement, suits most turntables, 10Hz-20KHz response (stylus $7.50) MCD SUPER QUALITY JELCO MC-140 magnetic cartridge with superb sound, 10Hz-27KHz response, 1.5-3 gms tracking, mounted on headshell for Japanese turntables (stylus $11.50)

$14

PRE-PAK ELECTRONICS

COMPARE THE VALUE!

QUALITY COMPONENTS

BONANZA

THINGS FOR DO-IT-YOURSELFERS

COMPARE THE VALUE! PRE-PAK ELECTRONICS

resistors

Range available:1ohm to 10megohms, 5% tolerance, multiples of - 10,12,15,18,22,27,33,39,47,56,68,82

QTY	1-9	10-24	25-99	100+
PRICE	3¢	2.5¢	2¢	1.5¢

Quantities can be mixed.

CAPACITORS

Greencap Plastic Film

50V rating - .001, .0015, .0022, .0033, .0039, .0047, .0056, .0068, .0082, .01, .015uF.....each 12¢
.022, .033, .039, .047, .056uF.....15¢
.068, .082, .1uF.....20¢
.15, .22, .33uF.....30¢
.47, .56, .68uF.....40¢
Buy 25 - less 20%, Buy 100 - less 30%

Ceramic Capacitors

1pF pref. values to 820pF ea.....8¢
.001uF pref. values to .033uF ea...9¢
.047uF...10¢ .1uF...14¢ .22uF...20¢

Tag Tantalum Capacitors

.1..22..33..47..68..1uF 35VW ea....35¢
2.2, 3.3, uF 35VW ea.....40¢
4.7, 6.8 uF 35VW ea.....45¢
10, 15 uF 25VW ea.....50¢
22uF 20VW....60¢ 33uF 16VW....65¢
47uF 16VW....70¢ 100uF 6VW....70¢

POTENTIOMETERS

SINGLE ROTARY POTS - LINEAR "A"
100,220,330,470,1K,2.5K
5K,10K,25K,50K,100K
250K,500K,1M,2M,5M, ea. 50¢

SINGLE ROTARY POTS - LOG "C"
1K,2.5K,5K,10K,25K,50K,
100K,250K,500K,1M ea. 50¢

SWITCHED ROTARY POTS - LINEAR "A"
1K,2.5K,5K,25K,50K,
100K,250K,500K,1M ea. $1.25

SWITCHED ROTARY POTS - LOG "C"
5K,10K,25K,50K,100K,
250K,500K,1M ea. $1.25

DUAL GANGED POTS - LINEAR "A"
10K,25K,50K,100K,250K,
500K,1M ea. $1.25

DUAL GANGED POTS - LOG "C"
10K,25K,50K,100K,250K,
500K,1M ea. $1.25
Buy 25-15%;Buy 50-15%;Buy 100-20%

TRIMMERS

MINIATURE PRESET POTS-LINEAR "A"
Smallest size, suits 0.1" grid PCB 100,200,500,1K, 2K,5K,10K,20K,50K,100K, 200K,500K,1M ea. 20¢

PRESET POTS-LINEAR "A"
Philips 0.25W rating
100,200,500,1K,2K,5K,10K, 20K,50K,100K,200K,500K,1M ea.30¢
Buy25-10%;Buy50-15%;Buy100-20%

Trimmer Capacitors

1.5-10pF plastic.....30¢
3-12pF plastic.....30¢
4-15pF plastic.....30¢
4-20pF ceramic.....45¢
5-30pF plastic.....35¢
8-50pF plastic.....40¢
5-50pF air-spaced..50¢
10-110pF mica.....45¢
12-115pF ceramic.....75¢
Buy 10-10%;Buy 50-20%;Buy 100-25%

Electrolytics

PRINTED CIRCUIT MTG

Note: Quantity Discounts May Be Mixed!

	Prices 16V	25V	50V
2.2 uF	12c	15c	18c
4.7 uF	12c	15c	18c
10 uF	12c	15c	18c
22 uF	12c	15c	20c
33 uF	15c	20c	25c
47 uF	15c	22c	28c
100 uF	20c	25c	40c
220 uF	33c	40c	60c
330 uF	35c	45c	70c
470 uF	40c	50c	--
1000 uF	60c	70c	--

PIGTAIL ELECTROS

	Prices 16V	25V	50V	63V
2.2 uF	15c	20c	22c	25c
4.7 uF	18c	20c	23c	30c
10 uF	20c	22c	25c	30c
33 uF	20c	25c	30c	35c
47 uF	20c	25c	30c	35c
100 uF	25c	30c	40c	50c
220 uF	50c	55c	70c	85c
330 uF	50c	60c	80c	$1.00
470 uF	70c	80c	95c	$1.20
1000 uF	75c	80c	$1.20	$1.50
2000 uF	90c	$1.40	$2.20	
2200 uF	63VW insulated can as			$2.50
3300 uF	100VW insulated can as			$4.75
4000 uF	75VW insulated can as			$5.50
4700 uF	35VW (rigid) as			$2.50

Buy 25. - 10%. Buy 50 - 15%. Buy 100. - 20%.

TRANSFORMERS

Model...	SAVE $$$
M-2851	6-3v-0-6-3v 150mA $2.90
M-2155	0-6-3,7-5,8-5,9-5,12-6,15v 1A $5
M-6672	0-15,17-5,20,24, 27-5,30v 1A WHILE STOCKS LAST $7

HIGH QUALITY-LOW PROFILE

8 or 14p.	5 for $1
16 PIN	4 for $1
18 PIN	3 for $1
24,28 P.	2 for $1
SOCKETS 40 PIN	1 for $1
14 PIN PLUG (Header)	5 for $1

DIL 1C

PCB ETCHING Kit

Includes Dala pen, 250ml ferric chloride, 3 PCB's, etch tank & instructions etc.

$4.99

SERVICE AIDS

SWITCH or CONTACT CLEANERS

Servisol ally spray 125ml for pots $2.50

Servisol evaporative spray 200ml now $2.50

KEYBOARD KITS

German 'Roti' high quality, Ideal for Keyers, Rotty lock System, Musicians or microcomputer type uses.

$5.50 4 Keys

0-9 and CLR Keys 18x18mm

NEW

AMP KITS from only $24.90

A small manufacturer found these U-beaut SINCLAIR Stereo 60 Pre-amps, chassis and hardware after stock-take. The pre-amp has ON-OFF switch, phono/tuner/aux inputs, VOL/BASS/TREBLE/BAL and runs on 9-40V DCat about 20mA. The chassis (all holes are punched) has labelled back panel with a separate satin aluminium front panel with black lettering.

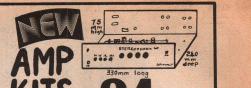

All This (worth $40) For $24.90

The A&R PT5755 transformer. 20-0-20v 1.5A gives 25-25V DC or 45-50v DC and will suit 15-50W AMPS. Transformer (worth $30) now $12.50.
Power Supply Parts (worth $5) only $4
The hardware for the chassis includes headphone socket, DPDT switch, 2 pin mains outlet, fuseholder & fuse, mains lead & clamp, spacers, screws and terminals etc (worth $10) only $6.

20W STEREO AMP

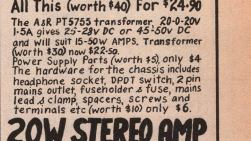

Reviewed in ELECT AUST. August '79

BASS, TREBLE, BAL, VOLUME
10W RMS in, 8-, 500mV input for Xtal or Ceramic cartridge, 0.5% distortion. AMPLIFIER ONLY $24.90 with wiring diagram etc. Spares available!

only $34 Complete with TRANS., KNOBS ETC.

TV CIRCUIT BOARDS

Over 80 parts incl. B trans. (2SC1419, 2SC711, 2SA673, 2SA628, 2SC620, 10 transistors, 2 FET pres, trimpots etc. etc.

$1.00 ea. or 10+ 80¢

PUSH-BUTTON TUNER BOARDS

current AWA TV sets

$3 EA for 10 OR $25

Comprisers 2 boards, one nas 8x DPDT push-button switches for 12chs/1st + similar 1x 100K multiturn trimpots with band-change switches.

LED DISPLAY PANEL FILTER

68mm x 38mm size

$2.95 EA.

BLACK PLASTIC FRAME WITH RED PERSPEX FILTER FOR LED DISPLAYS - ALSO INCLUDES MOUNTING KIT - REAL VALUE WORTH TWICE THIS SPECIAL PRICE BUY 10+ $2.50 ea. 100+ $2.25 ea.

Good things come in this little parcel

Jackpot No 4 $15

SPECIAL OFFER

Our latest assortment of over 100's of specials, samples, end-of-line closeouts, manufacturers over-runs etc. Jackpot No4 has all new items - contents vary, but contains not less than 3 Kgs weight. Add $4.15 for

TER BOARD

Project cost: $2.50

After building project five.

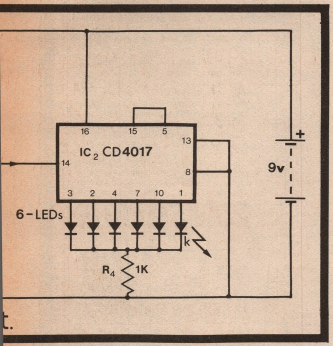

Parts list:

R1	resistor	10M	¼watt
R2	"	10M	"
R3	"	10k	"
R4	"	1k	"
C1	electrolytic	1mfd	16v
C2	capacitor	100n	100v
Q1	transistor	BC 557	
IC_1	timer IC	NE 555	
IC_2	decade counter	CD 4017	

LED_1 - LED_6 Large Red LEDs

battery clip
9v battery
approx 30cm hook-up wire

"Experimenter Board 3-ICs"

Building the circuit:

The idea behind this progressive series is to add to each of the previous projects to make a more complex project. This way you will be adding a minimum of components and building new ideas at the least expense. Remove the HEADS and TAILS LEDs from the previous project and all the other parts which will not be needed. Notice that some of the wiring will remain in place so refer to the layout diagram before starting. Fit the six LEDs in the centre of the board as shown. They will need connecting wires to the output pins of the CD 4017 so follow the layout diagram carefully. Solder the other components in place and re-check all wiring. Connect the battery and the circuit will come on with one LED illuminated. Touching the TOUCH PLATE will cause the LEDs to flash at a very fast rate and gradually slow down with just one of them lit.
We claim that the circuit is unbiased. But don't take our word for it. Complete your own statistical analysis of the circuit by taking 100 samples and putting the results in the following table:

No:	Count:	Total
1		
2		
3		
4		
5		
6		

Each time the LEDs stop, place a stroke in the appropriate space thus: / after each four strokes: //// the fifth stroke is placed across the four thus: 𝍸 This makes the final counting easy as they are now in groups of five. Look at your results. Are the totals of each LED nearly the same?
In an article to be presented in a few months, we will be adding a couple more components to this circuit and presenting it as a complete project on a printed circuit board. So wait for it.

LED DICE

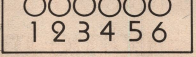

or

LED DICE

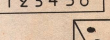

"Cut-out" display cards

TV Servicing

WHAT MULTIMETER?

These articles come from a practicing TV technician and revolve around TV problems. But they apply equally to any type of servicing such as amplifiers, CB or car radios.

The first worry for anyone wishing to start in the field of repairing is "What multimeter should I buy?"

I will answer this with 3 true stories on multimeters.

On my first day in a service work-shop I met a technician named Graham. He was the most incredibly capable technician I have ever known and the most amazing. Never once in the two years I knew him, did he ever use any test equipment what-soever. (I must add it was in the days of black and white valve sets). He preferred only bench work and you will see why. A set would be brought to him and in a flash the back would be off, the chassis lifted out and put on test leads. We extended his ability a bit on each of his jobs because the sets we gave him were genuine work-shop jobs in which the road technicians had tried all the valves and searched for any obviously burnt out parts. Within a short time Graham would say "that's it" - up would come the picture for an instant and he would pull his hand out of the TV. His secret repair tool was his two fingers! He would feel around the boost section locate the high voltage resistors and bridge each one with his fingers to create approximately the same resistance as the burnt out resistor and so the height would be restored. In a similar manner he would locate faulty or leaky capacitors in the sync section or vertical linearity and say "replace this one, this one and this one..." Invariably they fixed the set. I used this method for nearly 10 years after that. It does work. You can adjust the resistance of your fingers from 500k down to less than 50k and simulate a leaky capacitor. If the picture fault worsens when you place them across a particular paper capacitor it should be replaced. If the picture develops another fault, the capacitor is possibly ok. (paper capacitors were the biggest culprits). I have never been quite as game with the high voltage side. I prefer to use a 2M2 resistor on test leads for this.

The second story comes from Bert...a TV tech living some 10 miles from me. He had just recently bought a 100k ohms per volt FET voltmeter and was using it on a Thorn valve TV which had a fault in the EHT section. He applied the meter to the grid of the 6GM5 valve and got a high positive reading. Naturally he thought the oscillator or output stages were at fault and spent many hours replacing every part in the two sections. Still the high positive reading persisted. At this stage he came to me with the set and proudly displayed his new meter. My first test was to check the grid voltage with my 20k ohms per volt meter. Sure enough it was correct at -35v. The fault was in a boost capacitor and the set was fixed in 5 minutes. Bert had learnt his lesson. He returned the meter the same day and bought a cheap $25 special! The meter was in fact picking up stray hum and EHT voltage from the EHT transformer. The meter was far too sensitive.

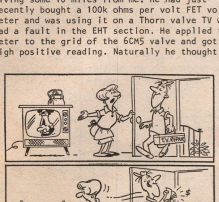

The third story comes from economics. The first meter I ever bought had a sensitivity of 1k ohms per volt. It lasted through 2 years of rough use repairing 100's of TV's before the needle began to stick. My next two meters were 10k ohms per volt. They lasted a few years also. I recently bought a taut-spring multimeter of 30k ohms/volt - it lasted one week and the movement siezed up. The core shifted and jammed the movement. It always happens. The expensive items get damaged first. I remember buying an expensive multimeter last year and dropped it within a month.

This all leads me to one conclusion. For repair work you only need two fingers - I mean a cheap multimeter in the price range $25 to $35. Sensitivities of 10k ohms/volt to 30k ohms/volt are quite satisfactory. Digital meters are an unnecessary luxury. Meters are bit like watches, who need to know the time to the second or a voltage of 35.05v?

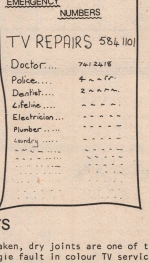

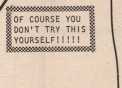

DRY JOINTS

Don't be mistaken, dry joints are one of the most prevalent single fault in colour TV servicing. They account for between 22-30% of all calls. Some TV sets ONLY suffer from dry joints. To back this statement may I say that to date I have never put a replacement part into at least two brands of colour sets. Their only fault has been poorly designed double sided PC boards which suffer from dry joints. The pin which connects the top track to the underside of the board tends to expand and contract during operation and eventually produces a dry joint.

This chapter reveals one of the most heavily guarded secrets of TV servicing. It is an insight for anyone wishing to take up colour servicing. Very little has been released in the past on dry joints mainly due to the difficulty in describing accurately their occurance and cure as told by an "old hand". Secondly, and possibly most importantly, their release has been avoided to prevent customers seizing the opportunity to express a little "knowledge" on a subject of which they know nothing.

...TV Servicing

There are five types of dry joints and five different attitudes to diagnosing them. A competent TV serviceman can be recognised by his approach to locating troublesome intermittent faults.
Here is a brief outline of how these dry joints occur and a proven method for locating them.

Some dry joints are classified as thermal faults. By this we mean the set will operate for a specific length of time then fail. This is due to the heat build-up in the set expanding the components and their leads a few thousandths of an inch (or even millionths of an inch) to create an opening or crack between the component lead and the PC board. This may result in the sound dying away or the picture closing to a line across the middle or both the sound and picture going off together. A bang on the back of the set generally restores full operation or alternately, turning the set off for half an hour will bring it back to life.

Believe me, finding intermittent faults is very time consuming and after many years on the road I have simplified the problem considerably. I let the customer do all the watching and testing. For two reasons I never take a TV out of the house. Apart from the damage caused to large sets in the transportation and the heavy lugging required, the real reason is that movement will generally heal the intermittent fault and it may take weeks for the fault to re-appear in the workshop.
"Soak Testing" a TV (watching the set with the back on) is very expensive and I have the sets generally do not fault in my work-shop! The second major point against removing a TV is the customer resistance. Most customers do not like their set removed from the house.

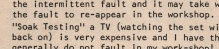

SO WHERE DO YOU START?

The following 5 points will help you diagnose intermittents on-the-spot but in most cases you will be guided 99% by past experience.

5 TYPES OF DRY JOINTS

1. An unsoldered joint. This is easy to spot. A component lead which has never been soldered on a PC board or tag strip is obvious. (I once fixed an unsoldered resistor attached to a tag strip on a 15 year old B&W set. It had faulted only after 15 years!) Use a hot iron when soldering the component to the board. Look for any other un-soldered connections.

2. Dirty Component Lead. The diagram shows a component which has not been pre-tinned and the solder does not "take" to the lead. The component should be removed, cleaned, tinned and re-soldered. If in doubt about the solderability of the lead, use a new component.

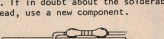

3. Hidden Dry Joint. In the diagram, the component does not pass through the board sufficiently to pick up the dip soldering process or the lead is dirty...creating a hidden dry joint UNDER a perfectly good external soldering connection. Moving the resistor will make it come away from the board.

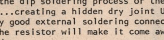

4. Heat or Excessive Current Failure. In this case the lead has been cut too close to the body of the resistor, allowing heat to flow into the solder connection, thus gradually destroying it and the surrounding PC board. If a fairly high current flows through the connection, the joint can develop heating troubles within itself, gradually failing and accelerating the process until finally burning itself out.

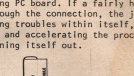

5. Expansion and Vibration Failure. Leads from transformers or coils can create very clean dry joints due to the high-frequency vibration of the transformer along with slight expansions and contractions, creating a pushing and pulling effect on the joint or joints until finally they become lose. This can also be due to insufficient solder forming the original

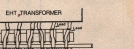

connection during dip soldering. Use plenty of solder when re-soldering and make sure the iron is hot.

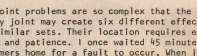

Dry joint problems are so complex that the same faulty joint may create six different effects on six similar sets. Their location requires extreme skill and patience. I once waited 45 minutes in a customers home for a fault to occur. When it did occur, I walked over to the set. This created enough vibration to fix the set for three days. (no, I'm not an elephant!) So how do you go about locating these faults? As I said, 99% is prior skill combined with lots and lots of LUCK. This is the skill part:

1. Inform the customer to turn the set on and have it faulting when you arrive at his home. You need to be promptly on the spot as some faults create excessive heating or even picture tube burn lines. Being on mobile 2-way is a great advantage. If a light tap on the cabinet remedies the problem - ask which side of the set responds best. A very light tap will mean the vibration created when taking the back off will heal it - so ask as many details as possible before leaving your workshop.

2. With the set still on, remove the back. If the set comes on, bad luck. Stop immediately and wait.

3. When the set does have a positive fault - place a large mirror a short distance in front of the screen so that it can be viewed from behind the set. When making any tests on the chassis such as tapping or freezing, you will need to look in the mirror constantly as it will be your certain guide to locating the vicinity of the problem.

...TV Servicing

4. Turn up all controls, including the colour to maximum. From the lack of picture and/or sound, you will need to divide the set into approximately four sections, something like this:

   Black screen and no sound - power supply or EHT section.
   No sound but picture ok - sound section.
   Weak snowy screen - tuner or IF strip.
   Black screen, sound ok - EHT section.

   The above is greatly simplified however you will need to ask yourself whether it is a power supply fault, sound fault, high voltage fault or tuner fault and concentrate on this particular section.

Each set differs as to fault locating and it would take 100 pages to list all the methods of attack. As a general rule, I use this method:

1. With the set still on, remove the back carefully. Use a can of "FREEZE" (compressed carbon dioxide) to spray accurately all over the PC board starting at one end of the soldered side and working systematically over the board. Cover every board in the set. Next spray each and every component with the CO_2. (I have never had it damage any components, even when it freezes them to almost absolute zero - but keep the nozzle a little distant from the parts all the same.
2. Obviously you have been inspecting the soldering while spraying. This time I suggest making a closer inspection - especially around the pins of EHT transformers, switch-mode-power-supply transformers and high wattage resistors. Look for any burn marks, unusual or poor soldering and re-solder any suspect connections. It is best to solder with the set off, so before making any repairs, switch the set off for 30 seconds then on again to see if the fault is self-healing. Once you are satisfied the set remains faulting you can re-solder a few connections at a time, then turn the set on.
3. Some faults do not respond to freezing or inspection. For these intermittent joints you will need low-level illumination and a plastic handled screwdriver. If the PC board is large and mounted on a thin frame it can be twisted by holding the upper and lower corners of the board. This is extremely dangerous because you are using two hands for this operation. Make absolutely certain that you are just touching the blank PC board or the metal frame-work as the grip you are applying will allow any voltage over 100v to become quite lethal. Twist the board quite noticeably and wait for any reaction. Quite often you will see a spark from the faulty joint and the set springs into life. The other approach is to tap the board with the plastic handle of the screwdriver and gradually home-in on the fault.

There is no other magic to finding dry joints. These are the general basic rules and provided you keep a mental record of each and every dry joint as you find it, you will build up a skill equal to any expert.

light the led *MODIFIED*

After a couple of requests for help with LIGHT THE LED, we found the de-bounce circuit comprising the two electrolytics at the input of CD 4017, was not good enough. Some brands of IC's were more sensitive and had a tendency to clock two or even three outputs on a single pulse of the switch. No matter how we altered the 2-capacitor de-bounce network, it was not satisfactory. So we designed a different arrangement. This time we employed a transistor to change the state of the input gate from HIGH to LOW. As the 4.7mfd cap charges, the base voltage rises, turning on and saturating the transistor. The voltage at the collector changes from rail voltage to about one volt. This clocks the IC. This circuit works with any CD 4017 and enables the led to light correctly every time. All the parts can be mounted on the PC board without cutting any copper tracks.

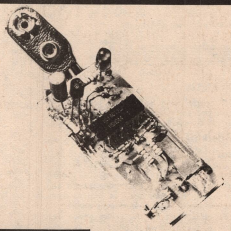

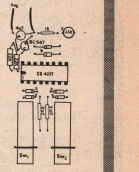

Light The Led (Modified)

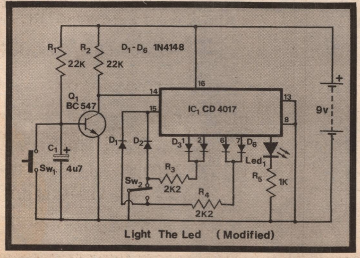

Light The Led (Modified)

Parts list:

2 - 22k ¼w
2 - 2k2 "
1 - 1k "
1 - BC 547
1 - 4.7mfd 10v
6 - 1N 4148
1 - Red 5mm LED
1 - CD 4017 IC
1 - Battery clip
1 - Springy brass strip

10-MINUTE DIGITAL COURSE

IN BLOCKS 1 → 16 WE SAW HOW AND OR NOT, NAND & NOR GATES FUNCTION.

THIS SECTION SHOWS HOW NAND & NOR GATES CAN BE USED IN FLIP FLOP CIRCUITS.

17. THE FLIP FLOP

* HAS 2 STATES: "0" & "1" OR "LOW" & "HIGH".
* CHANGES STATE VERY RAPIDLY.
* CAN HOLD "A PIECE OF INFORMATION".

A SIMPLE FLIP FLOP – CONNECT 2 NOR GATES:

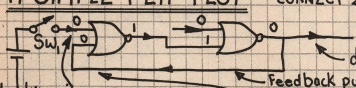

1. INITIALLY THIS GATE HAS "0" ON IT.
2. LET US ASSUME THE BOTTOM INPUT IS ALSO "0".
3. THE OUTPUT OF FIRST NOR GATE WILL BE "1".
4. THE INPUTS TO THE SECOND NOR GATE WILL BE "0" & "1".
5. THE OUTPUT OF THE SECOND NOR GATE WILL BE "0"
6. THIS OUTPUT FEEDS BACK TO THE FIRST NOR GATE.

ON CLOSING SWITCH SW_1:

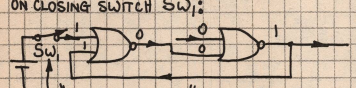

1. THE SWITCH GIVES A "1" TO THE TOP INPUT GATE.
2. A "0" & "1" ON THE INPUTS MAKES THE OUTPUT CHANGE TO "0"
3. THE SECOND NOR GATE HAS "0" & "0" ON ITS INPUTS, MAKING THE OUTPUT CHANGE TO "1".
4. THIS "1" FEEDS BACK TO THE FIRST NOR GATE.

ON OPENING THE SWITCH SW_1:

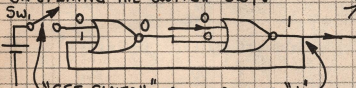

* WHEN SWITCH SW_1 IS OPENED THE FIRST NOR HAS "0" & "1" ON ITS INPUTS. THE OUTPUT DOES NOT CHANGE.

THUS WE HAVE REGISTERED:

"A PIECE OF INFORMATION".

18 TO "RESET" THE SIMPLE FLIP FLOP BACK TO ITS ORIGINAL STATE WE NEED A SWITCH AT THE SECOND NOR GATE.

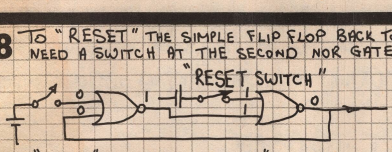

THE "RESET" SWITCH PUTS A "1" ON THE TOP INPUT OF THE SECOND NOR GATE. THIS CHANGES THE OUTPUT TO "0". THIS FEEDS DIRECTLY TO THE INPUT OF THE FIRST NOR GATE, AND CAUSES ITS OUTPUT TO CHANGE TO "1". THIS CREATES A HIGH ON BOTH INPUTS OF THE SECOND NOR GATE.

ON OPENING THE "RESET" SWITCH:

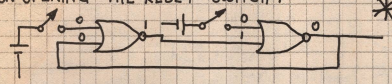

* WHEN THE "RESET" SWITCH IS OPENED THE OUTPUT DOES NOT ALTER & THE RESET SWITCH HAS NO FURTHER EFFECT.

A CMOS CD4001 IC CONTAINS 4 NOR GATES. WE CAN USE ANY TWO OF THEM TO MAKE A FLIP FLOP:

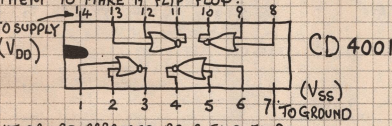

CD 4001 IS A QUAD 2-INPUT NOR GATE.

IT CAN BE ARRANGED AS A FLIP FLOP:

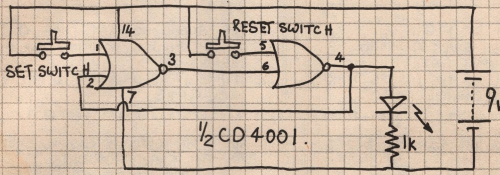

CLOSING THE "SET SWITCH" WILL TORN THE LED ON AND THE "RESET" SWITCH WILL TURN THE LED OFF

A FLIP FLOP CIRCUIT IS A BASIC BUILDING BLOCK. IT IS REDRAWN IN #19 WITH A SINGLE SWITCH. THE NEW LAYOUT WILL BE EASIER TO UNDERSTAND & FOLLOW.

19 NOR GATE FLIP FLOP:

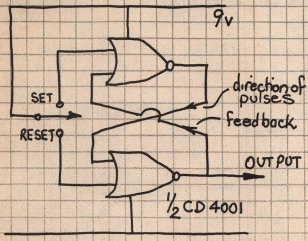

NAND GATE FLIP FLOP

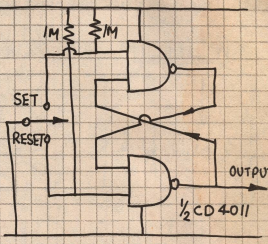

THE FIVE LOGIC FUNCTIONS:

AND
OR
NOT
NAND
NOR

CAN BE PERFORMED BY CD 4001 & CD4011 IC's.

1. AND

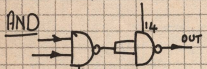

Using a CD 4011 as an AND gate

2. OR

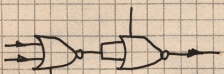

USING A CD 4001 as an OR gate

3. NOT

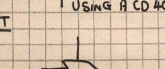

USING A CD 4001 AS A NOT.

4. NAND

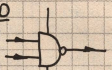

A CD 4011 IS a NAND GATE

5. NOR

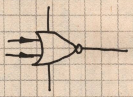

A CD 4001 IS A NOR GATE

The most useful IC's are NAND & NOR gates. They can arranged to perform all the five basic functions.

With their inverting outputs we can build them into a number of clever switching and latching circuits. These will be described in the next sections.

20 Since SOME PULSES IN ELECTRONICS ARE ONLY PRESENT FOR VERY SHORT PERIODS OF TIME, WE MUST HAVE SOME WAY OF STORING AND RECORDING THEM THE ANSWER IS.....

.... A LATCH — A CD 4001 OR CD 4011 CAN BE USED AS A LATCH.

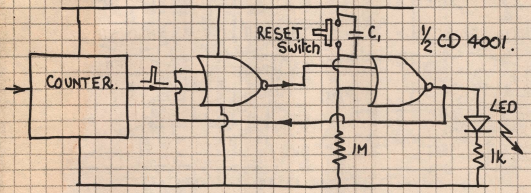

THE OUTPUT OF THE COUNTER IS NORMALLY "LOW". IT GOES "HIGH" FOR 1 PULSE THEN LOW. THE LED WILL LIGHT & STAY LIT. IT WILL "LATCH ON". THE RESET SWITCH WILL TURN LED OFF.
THE CIRCUIT HAS INDETERMINATE START-UP. BUT WITH C_1 THE CIRCUIT WILL START UP WITH THE LED OFF.

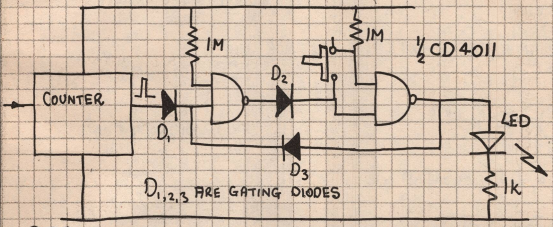

DEBOUNCE SWITCH:

Whenever a mechanical switch is included in a digital circuit there will be problems of "SWITCH BOUNCE". This is due to the contacts striking each other several times before finally closing. Since ICs such as counters and flip flops will record frequencies up to many MHz they will register the opening and closing of a normal switch as several pulses and produce a false reading. To eliminate this problem we can use two NAND gates to form a DEBOUNCING CIRCUIT. In this type of circuit, the states are unaffected by noise, since the states are changed by the first noise pulse from the switch and cross-coupling causes the circuit to self-latch and be immune to further pulses.

21 .....DEBOUNCE SWITCH.

THE IMPORTANT POINT TO NOTE IS THE IC DOES NOT CHANGE STATE ON OPENING THE SWITCH CONTACTS, NOR DOES IT CHANGE STATE ON RE-CLOSING THE CONTACTS BACK TO THE SAME GATE.

USING A CD 4001 NOR GATE:

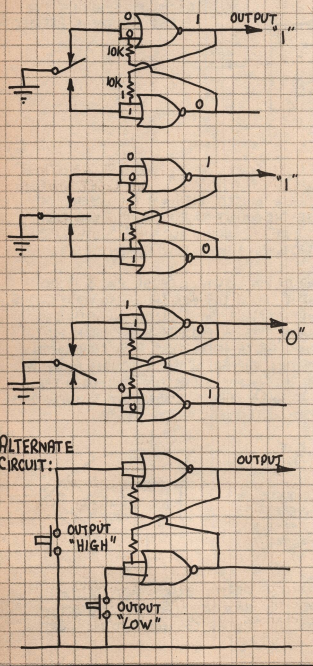

USING A CD 4011 NAND GATE:

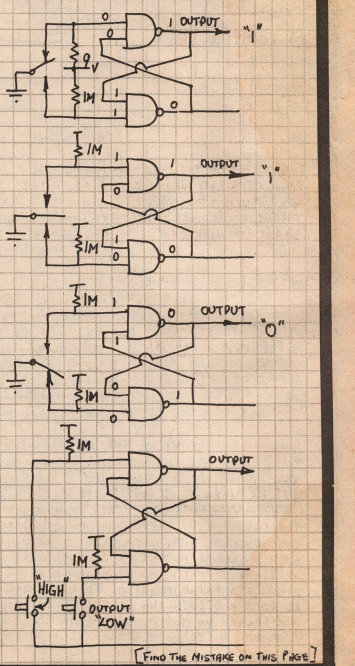

[FIND THE MISTAKE ON THIS PAGE]

22 MULTIVIBRATORS:

THE MOST USEFUL MULTIVIBRATOR IS THE ASTABLE OR SQUARE-WAVE GENERATOR. THE CIRCUIT SHOWS ½CD4001 IC USED TO MAKE A 1KHz ASTABLE MULTIVIBRATOR.

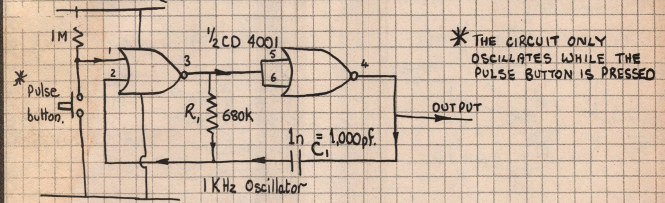

HOW THE CIRCUIT WORKS:

THE CIRCUIT IS SHOWN GATED OFF DUE TO PIN 1 BEING BIASED HIGH VIA THE UPPER 1M RESISTOR. [A HIGH ON EITHER INPUT GATE WILL CAUSE THE OUTPUT TO GO LOW.] THUS PINS 3,5&6 ARE LOW. PINS 5&6 ARE THE INPUT GATES OF THE SECOND NOR GATE AND WILL CAUSE THE OUTPUT PIN 4 TO BE IN A HIGH STATE UNTIL PIN 1 GOES LOW MOMENTARILY.

WHEN A PULSE OF SHORT DURATION IS DETECTED ON PIN 1 IT WILL CAUSE PIN 3 TO GO HIGH AND THE OUTPUT PIN 4 TO GO LOW. SEE TRUTH TABLE FOR NOR GATES TO VERIFY THIS. CAPACITOR C_1 BEING FULLY CHARGED, WILL ATTEMPT TO MAKE PIN 2 SWING NEGATIVE WITH RESPECT TO THE 0v RAIL. LET ME EXPLAIN THIS IN ANOTHER WAY WHICH MAY BE EASIER TO UNDERSTAND. SUPPOSE WE CONSIDER THE CAPACITOR TO BE A 9v RECHARGEABLE BATTERY. INITIALLY THE BATTERY IS IN A STATE OF FULL CHARGE. WHEN A TRIGGER PULSE IS RECEIVED AT PIN 1 THE FIRST NOR GATE WILL GO HIGH AND SINCE IT IS DIRECTLY COUPLED TO THE SECOND NOR GATE IT CAUSES THE OUTPUT PIN 4 TO GO TO 0v. THIS IS EQUIVALENT TO UNPLUGGING THE FULLY CHARGED BATTERY AND PLACING ITS POSITIVE TERMINAL ON THE 0v RAIL.

IN BUILT INTO EACH GATE OF THE IC ARE 3 DIODES, ONE OF WHICH PREVENTS THE INPUT SIGNAL GOING BELOW 0v (the other two are discussed later). SO WHEN THIS -9v IS PRESENTED AT INPUT GATE 2, DIODE D_3 CONDUCTS VIA THE 1k RESISTOR AND QUICKLY REMOVES THE CHARGE ON THE CAPACITOR (OR BATTERY ANALOGY). WITH THE CAPACITOR FULLY DISCHARGED, IT BEGINS TO RECHARGE IN THE REVERSE DIRECTION FROM THE HIGH ON PIN 3, VIA R_1 AND THE VOLTAGE ON PIN 2 STARTS TO RISE EXPONENTIALLY TOWARDS THE POSITIVE RAIL. DURING THIS RISE THE TRANSFER VOLTAGE IS ATTAINED AND CAUSES THE OUTPUT PIN 3 TO GO LOW AND PIN 4 TO GO HIGH.

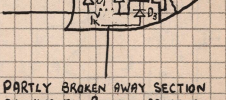

PARTLY BROKEN AWAY SECTION SHOWING THE 3 INPUT PROTECTION DIODES CONNECTED TO EACH GATE.

TEST YOURSELF... No 2

How good are you at identifying capacitors? This quick test will give you a rating.

CAPACITORS ..

Capacitors come in so many shapes and sizes. They have at least 3 different identification codes and sorting them out can be quite difficult. This can be a problem as their size bears no relationship to their value, rating or type of constructional material. So let's see how much you know....try this test and give yourself a rating. The marks for each question do not relate to their difficulty.

1. Name 5 types of capacitors:

   A: (No cheating now)

   B:

   C:

   D:

   E: (10)

2. Draw the symbol for:
   (a) A capacitor:

   (b) An electrolytic:

   (c) A variable capacitor:

   (d) A non-polar 10mfd electro:

   (8)

3. Explain with words or a drawing:

   (a) green cap:

   (b) PC mounting:

   (c) RT or PT leads:

   (d) "styro":

   (e)

   (f) "poly":

   (8)

4. Arrange these capacitors in approx order of size: small,med,large:

   (a) 1mfd 63v ceramic.....( )
   (b) 1mfd 63v electrolytic..( )
   (c) 1mfd 63v paper.....( )
   (d) 1 mfd 63v polyester....( )
   (e) 1mfd 63v tantalum.....( )

   (3)

5. List all the values of capacitors between .001mfd and .027mfd:

   (16)

6. Can you give a simple explanation why these three electrolytics will be about the same physical size:

   1mfd 350v
   10mfd 35v
   100mfd 3.5v

   (2)

7. An electrolytic can suffer from at least 3 main faults. Can you name them:

   (a)

   (b)

   (c) (3)

8. Draw:

   (a) 2 capacitors in series:

   (b) 2 capacitors in parallel:

   (2)

9. Almost any value of capacitance can be created by joining caps in series or parallel or a combination of both. In addition, high-voltage ratings can be achieved with this method.

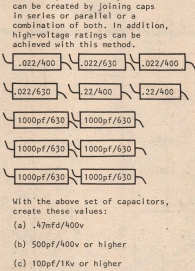

   With the above set of capacitors, create these values:

   (a) .47mfd/400v

   (b) 500pf/400v or higher

   (c) 100pf/1Kv or higher

   (d) .01mfd/1Kv or higher (8)

10. When choosing an electrolytic, why should its rated voltage be close to its working voltage?

    (2)

11. What is the advantage of a tantalum (and the new tantalum equivalent) over ordinary electrolytics?

    (4)

12. Would you use a ceramic capacitor as a timing capacitor? (the frequency setting capacitor in an oscillator circuit)

    (2)

13. What is the value of these combinations:

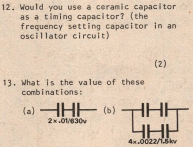

    (8)

14. Explain the fault with these arrangements:

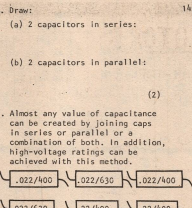

    (4)

Total: 80marks.

Answers:

1. Paper, Ceramic, Polystyrene, air, Polycarbonate, Polyester, Electrolytic, Tantalum, Mica.

2. 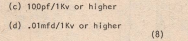

3.(a)the name given to a style of polyester capacitor using green resin coating. (b)Printed Circuit Mounting with both leads at one end.(c)Rat Tail, PT=Pig Tail - where one lead emerges from each end. (d)Polystyrene (e)N:style number which does not involve us. 630:the working voltage .68:the capacitance in mfd K:tolerance which is ±10% (f) Polypropylene or polyester. 4.Approximately the paper will be the largest,then polyester,ceramic,electrolytic and tantalum the smallest. 5..0012,.0015, .0018,.0022, .0027, .0033, .0039, .0047, .0056, .0068, .0082, .01, .012, .015, .018, .022. 6. A factor obtained by multiplying the capacitance and the voltage will give the size of an electrolytic. 7. Drying out and losing capacitance, intermittent connections to the leads, shorting internally, open circuit.

8. (a) (b)

9. (a)Two .22mfd in parallel. (b)Two 1000pf/630v in series. (c)

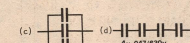

10. To keep the electrolytic"formed" 11.smaller size, lower leakage current. 12.No,never. 13.(a)4n7/1kv (b)2n2/3kv (c)33n/400v (d)12n/2.5kv 14.The capacitance is correct but the voltage will be equal across each capacitor so that 1kv will appear across the 630v cap. (b)The cap is correct but the voltage rating of the combination is still 630v. Thus 2kv will appear across the 630v capacitors.

score:

Over 70 marks	-	Excellent
over 60	-	Very Good
over 50	-	Good
below 50	-	Not a pass

THE TRANSISTOR PAGE

"So? What's the trick?" you ask. "The circuit looks perfectly normal to me".

When you build up the circuit you will find the switching plate, called a TOUCH PLATE, has only ONE wire connecting it to the circuit. Now anybody with even the slightest idea of electrical circuits knows you need two wires for a switch to operate. Thus the trick. We need only ONE wire!

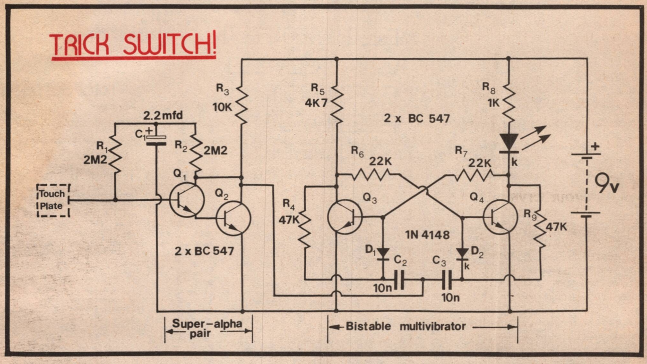

Unfortunately nearly everyone also knows about touch controls. We see them in lifts and touch pads to open doors so the day may be nearly past when a one wire touch switch has any real impact. Anyway it does provide a neat project with potential for experimenting and you may find a new use for a touch plate in the process.
This circuit does not have a "one touch and it's on" or "one touch and it's off" ability as the random chance of the LED finishing up lit is 50%.

HOW IT WORKS:

The TRICK SWITCH uses 4 transistors to create two individual building blocks.
The first two transistors form a DARLINGTON PAIR (super-alpha pair) in which the gain of the circuit is very close to the product of the two transistors. When you touch the TOUCH PLATE with your finger, your body is acting like an antenna, picking up stray hum similar to the noise you get when you touch the input of am amplifier. This 50Hz hum is amplified sufficiently by the two transistors to trigger the second section.

Transistors Q_3 and Q_4 make up the second building block and form a BISTABLE SWITCH or BISTABLE MULTIVIBRATOR. This means it has two states and requires triggering into each state. This circuit does not possess any frequency of its own but will flip from one state to the other at a rate determined by the pulses arriving at C_1,C_2. A red LED provides the load for transistor Q_4 and when the TOUCH PLATE is touched with your finger it will start the LED flashing at about 25Hz or so according to the frequency of the stray hum. When your finger is removed the LED will immediately settle into one of its two conditions. Either fully 'ON' or fully 'OFF'. Since the components surrounding Q_3 and Q_4 are of equal value, the chance of the LED remaining lit is 50%.

To provide guaranteed triggering for the bistable section, two steering diodes are included. Their operation is as follows: Suppose the circuit is in one of its two stable states with Q_3 cut-off and Q_4 conducting. This means that diode D_1 will have a positive voltage on its cathode via R_4 and R_5 and the anode will be brought to ground via the 22k resistor R_7. This diode will be reverse biased. Diode D_2 will have its cathode near ground potential via the 47k resistor R_5 and its anode near positive potential via R_6 and R_5. This diode will be forward biased. The placement of the two steering diodes makes them only capable of turning off their respective transistor. This means that the next pulse appearing through capacitor C_2 can have no effect on transistor Q_3 since it is already cut-off but a negative-going

pulse through C_3 will remove the forward bias on Q_4, via diode D_2, and turn off the transistor. The voltage on its collector will rise and turn on Q_3. Thus the circuit will change state sharply and remain in this state until a suitable negative-going pulse causes it to "flop".

CONSTRUCTION:

The circuit contains no critical-value components and almost any NPN transistors will be suitable. The resistors need not be the exact values shown in the diagram. You can use any value resistor either side of the one specified provided you keep the symmetry between the two bistable multivibrator transistors so that the "mark-space" ratio will be equal and the chance of the LED being left illuminated kept at 50%.

Build the circuit on a small piece of veroboard. A handy size to buy is 15 holes x 81 holes which can be cut to length for a number of different projects. If you lay out the parts carefully, you will not have to cut any of the copper tracks; a very awkward and messy operation if you don't have the spot-face cutter.

Footnote:

Actually the TRANSISTOR PAGE is designed to highlight the inefficiency and complexity of building circuits with transistors. This TRICK SWITCH is a perfect example. The same effect can be performed with one simple 50c IC and just 7 external components! Consider the speed in assembling 8 parts compared to the TRICK SWITCH circuit with its array of transistors, resistors, diodes and capacitors.

Hopefully you will be gradually weaned off transistor projects and onto "little black packages". For the moment we will use the TRANSISTOR PAGE projects as an insight into the operation of various modules or building blocks. Consider them purely as this. Any circuits you wish to build should utilize spare or used components to keep construction cost to a minimum and justify their assembly.

AMPLIFY!

your crystal set

Build this simple two transistor amplifier for your crystal set and pull in the weaker stations. This circuit will operate with almost any type of transistors and will surprisingly still keep functioning when the battery is dis-connected. Since it takes so little power we have not included a switch. When the power is applied, the transistors amplify the signal considerably and you may even be able to drive a small 15ohm or 33ohm speaker if the voltage is increased to 6v.

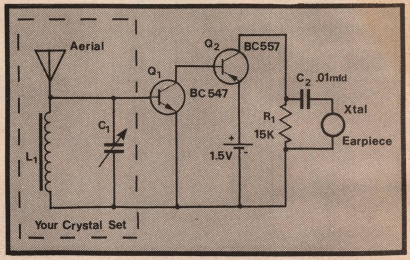

Almost any crystal set can be used. The only part you need to remove is the crystal itself. Its function is performed by the first transistor. Crystal sets can be roughly divided into two groups. Slug tuned coil types and variably capacitor types. The first has a coil of wire wound on a former in which a ferrite rod is allowed to slide. This rod varies the "Q" of the coil and thus alters the frequency at which the circuit will resonate. This coil is used in conjunction with a fixed capacitor of about 400 - 500pf. Unfortunately the effectiveness of this circuit diminishes as the rod comes out of the coil. This is overcome by having a fixed aerial coil& rod assembly and adjusting the capacitance in the circuit. Open up your crystal set and take a look inside. It will not matter which type you have. They will both work equally well with this high gain amplifier. All the parts will fit inside the crystal-set container without the need of a tag strip. Try to make a neat "birds-nest" soldering job.

Good Luck!

transistor offer:

Please send 1 pack of 20 transistors @ $2.40 plus 60¢ post to:

NAME_ _ _ _ _ _ _ _ _ _ _ _ _ _ _ _ _

ADDRESS_ _ _ _ _ _ _ _ _ _ _ _ _ _ _ _ _

_ _ _ _ _ _ _ _ _ _ _ P/code_ _ _ _ _

I enclose cheque/postal order for $3.00

Send to: TALKING ELECTRONICS MAGAZINE
35 Rosewarne Ave.,
Cheltenham, 3192.

Coupon not essential in some states of Aust. for this offer.

EXPERIMENTER DECK

HEADS or TAILS?

PROJECT TWO

This project adds a further 9 parts to the HEE HAW SIREN to make our 2-LED readout "HEADS OR TAILS". You must complete the HEE HAW first and have it operating correctly before starting this project. This way you are testing your workmanship in stages...its no good completing a project to find it doesn't work.

THE ORIGIN OF HEADS OR TAILS

In days gone by, players would toss a penny to see who would commence playing a game. This custom is still carried on in cricket. When pennies were in full circulation, one of the simplest games in the world used a penny as the sole betting medium. Although highly illegal, groups or sharp, daring punters would gather behind deserted buildings to play what they called "the fairest game in the world"...TWO-UP. It consisted of tossing a penny in the air and while it is spinning high above their heads, a punter would place a bet on it landing on the ground either heads or tails. A penny was used not only for its large size but because they knew the chances of it landing heads was exactly 50%.

Since there aren't any pennies around today, (and 20c coins are just "not the same") you can make your own heads or tails predictor with the aid of electronics and learn about the laws of chance.

PARTS

R5	Resistor	10K
R7	"	4K7
R8	"	4K7
R9	"	120R
2 -	5mm Red LEDs	
2 -	diodes	IN 4148
IC_2	CD 4017	
5 -	Molex pins	

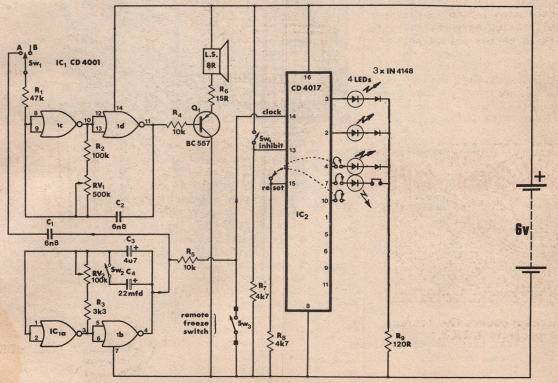

fig.2&3 HEADS or TAILS - use 2 LEDs
DECISION MAKER - use 4 LEDs

This circuit is designed to have no bias, meaning it doesn't tend to favour one LED or the other. This means it can be used with confidence, which is more than could be said about the reliability of a "TWO-UP SCHOOL"...as they used trick pennies, and fluttering instead of spinning the coin!

MOUNTING THE PARTS

Solder the CD 4017 carefully onto the board with pin1 passing through the correct hole. Use your fingers as a heat-sink. Follow the layout diagram to locate the positions of the 4 resistors, 2 LEDs and 2 diodes. The LEDs and diodes must be inserted around the correct way or they will not operate. Don't heat up the LEDs excessively while soldering as this will destroy their brightness. Make up 4 jumper leads from 5cm lengths of hook-up flex. Tin both ends of each lead and solder them in positions marked "U". On the jumper lead nearest the CD 4017, solder a flying Molex pin to the lead. Fit a Molex pin to the PC board in the three positions shown. Cut two short resistor leads and insert them into the board in positions marked "W". The flying Molex pin will fit onto either of these wires to form Sw4, the clock inhibit switch. For projects 2 & 3 it is moved from wire W_2 to W_1 to freeze the output.

For project 2 the reset jumper J_4 is connected onto the Molex pin near IC_2. This will allow only the first two outputs to become activated.

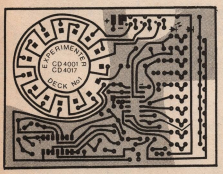

Shaded area covers the soldering for projects 1,2&3.

HOW THE CIRCUIT WORKS

The CD 4017 is a counting IC. We are using only two of its outputs in this project. The first output is pin 3 and the second output is pin 2. It has a further 8 outputs which are not used in this project. They are by-passed by using the reset pin number 15 as follows: The third output pin 4 is connected back to the reset pin so that the IC will clock from pin 3 to pin 2 then back to pin 3 again.
The input pin 14 counts the incomming pulses from the flip-flop $IC1_a$ and $IC1_b$. By rotating R_2 to minimum resistance the frequency will be about 24Hz. This is the highest frequency obtainable from the flip-flop. Its range starts from one cycle per 9 seconds to 24 cycles per second. The counting IC accepts this and displays the pulses alternately at pins 3 and 2. This means each LED will flash at 12 times per second In fact it will look as if both LEDs are glowing dimly. The IC has another feature built into it at pin 13. This is called the "clock inhibit" pin. Its function is to "freeze" the output at any given instant. It comes into operation when a voltage above about 4v is applied to pin 13.
To obtain positive freezing or clocking we apply either full rail voltage or zero voltage to this pin. In this project we use this "freezing" facility to give us a readout of either heads or tails. At the rate of 12 flashes per second you will be unable to deliberately stop the motion of a particular LED due to the cycling being higher than the Persistence of Vision. (Which is about 5-6Hz). Thus the freezing of either LED will be completely at random and since both LEDs are clocked on and off at an equal rate, (50% duty cycle each), there will be no bias towards either.

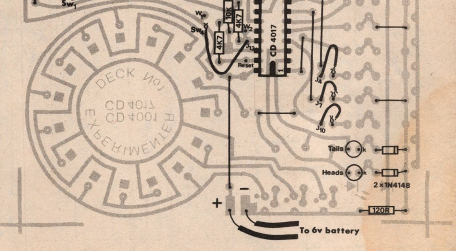

HEADS OR TAILS LAYOUT

DECISION MAKER

PROJECT THREE

This is a simple extension to HEADS or TAILS. It uses the first four outputs of the IC. At the moment this project may not seem very exciting. Mainly because we have not high-lighted it but it must have appeal in the community as 100's of Decision Makers have been sold @ $29.95. Why would you buy a decision maker? Possibly because we all like decisions to be made for us. Especially when the decision is favourable. That's why you'll like this project. On the surface it looks like an ordinary four-readout display and you would think it gave you a 50/50 chance of arriving at a favourable decision. But on closer inspection you find you have only 25% chance of landing on the LED marked "DO IT NOW". The more alternatives that are provided in the readout will lessen your chance of being stuck with the task.

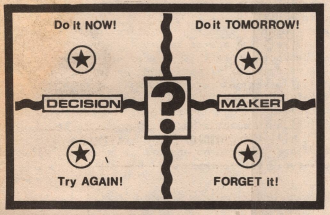

Use this DECISION MAKER display card if you intend to build the project permanently in a zippy box. The LEDs fit in the centre of each quadrant. In a future issue a special printed circuit board will be designed to fit below the display to produce a smaller and neater project. An on/off switch would need to be included in the circuit to conserve the battery.

DECISION MAKER PARTS

ADDITIONAL PARTS NEEDED

2 5mm LEDs

1 diode 1N 4148

MOUNTING THE PARTS

The three parts are mounted in alignment with the other two LEDs. The reset jumper J_4 is returned "home" and J_{10} is used as the reset jumper.

HOW THE CIRCUIT WORKS

As mentioned before, the CD 4017 is a counting IC. This time we are using four of its outputs. It will clock each of these in turn allowing the 24Hz incomming frequency to be evenly distributed between the outputs to register six cycles per second on each LED. This frequency is sufficiently low enough for you to be able to see slight flickering, however you will not be able to stop the motion on a particular LED. To freeze the LEDs you will need to move the clock inhibit jumper SW_4 from W_2 to W_1. This will stop the motion instantly. Whether you go by the decision of this game will reflect your acceptance of "things electronic". You will always be able to come back to this game after completing the 10 projects.

DISPLAY CARD

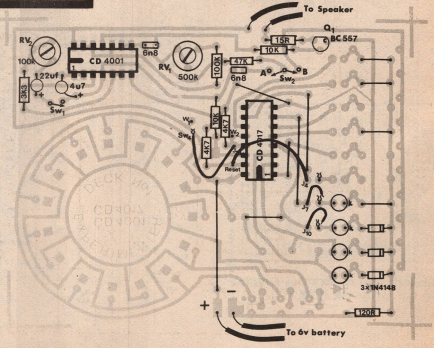

DECISION MAKER LAYOUT

RUNNING LIGHT

PROJECT FOUR

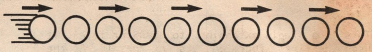

PARTS

5 - 5mm Red LEDs
1 - 5mm Green LED

3 - IN 4148 diodes

The RUNNING LIGHT project shows the full sequence of the CD 4017 counter. It uses all the 10 outputs to drive 10 LEDs. The IC turns each output on and off in turn to give the effect of a RUNNING LIGHT. Depending on the frequency of the incomming signal, the light will seem to travel at varying speeds. In a darkened room, this effect is most interesting. After watching it for some time, you will be quite convinced a single LED is moving across the PC board. Our eyes are wonderful image-makers. An old saying goes "Believe nothing of what you hear and only half what you see", holds true for this effect.

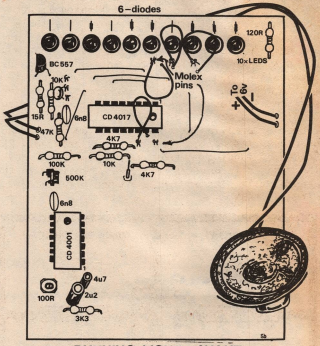

RUNNING LIGHT LAYOUT

MOUNTING THE PARTS

The 6 LEDs and 3 diodes are connected in alignment with the 4 LEDs from the DECISION MAKER project. All the jumper leads should be "home" to allow the IC to clock the full 10 outputs. If you have one green LED, it should be positioned as LED number 9 as the next project uses it to record a score or "hit".

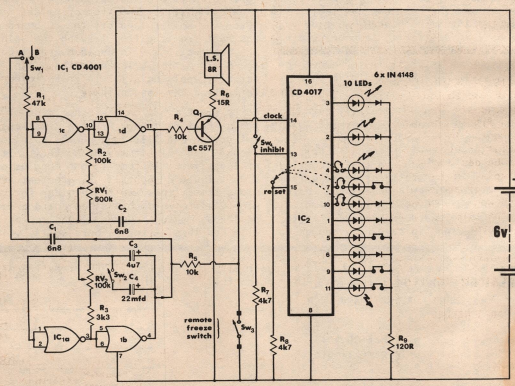

The idea behind this project is to give the constructor (that's YOU!) a starting-point for additional experimenting. I wouldn't put the RUNNING LIGHT project away until I had extended its function to say 2 CD 4017's or even putting 40 LEDs in series-parallel to make a square 10 LEDs by 10 LEDs. An even more exciting display combines 2 rows of 10 LEDs wired in opposite directions. The variations are enormous.

Anyone creating a visually exciting or tricky display is invited to send it in for publication. This would fit in ideally with our format. We like to keep extending our projects as this is the most economical approach to circuit construction.

Keep the remainder of the kit of parts for the next episode...to be released next issue.

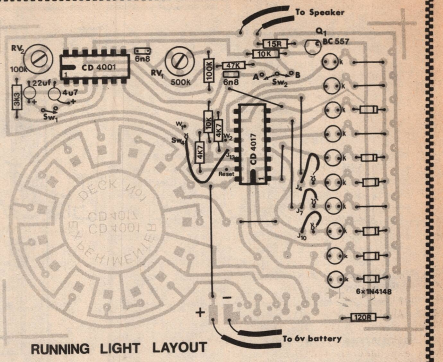

RUNNING LIGHT LAYOUT

Removing IC's...

One day the time will come when you want an IC for a new project and the only one available will be firmly soldered into a PC board. What do you do? You don't have a desoldering iron or solder sucker or even de-solder wick. It may seem an impossible task but it is possible to remove the IC without completely over-heating it so that it can be re-used.

Unfortunately, in the process, you will ruin the PC board but that's preferable to overheating the chip, or not getting it at all.

Firstly you will need a small piece of ALFOIL to fit tightly over the IC and short all the pins together. This will stop static or leakage from the soldering iron affecting the input gates. It's best to mount the PC board in a clamp or holder because you will need both hands free to work on the de-soldering. Surprisingly enough you will need some solder for the task. I also suggest a constant-heat soldering iron and definitely not a "quick-heat" type as you will tend to overheat the joint in your enthusiasm to get the job done quickly. Begin at pin one with the soldering iron and small screwdriver or pliers. Carefully lever the solder land off the PC board with driver and heat from the iron leaving the pin free of any obstructions. To avoid overheating the IC, the maximum time allowed for each pin is 4 secs. Actually applying a little fresh solder will aid in lifting the land quickly.

Next select a pin on the other side of the IC to reduce heat build-up. After a great deal of careful prying and lifting you will gain yourself ONE second-hand IC! It may be worth it, it may not. At least you will come to one conclusion. Why didn't I use a socket! My greatest achievement along these lines was to desolder forty-seven 16 pin IC's from a **double-sided** board programming a paper-bag making machine....and replacing them with NEW IC's. After 4 hours solid....it worked!

Quiz:

For the first time, can you see yourself really getting somewhere with electronics?

1. Draw these gates: NAND, OR, NOT, AND, NOR.
2. Explain: V_{SS} V_{DD}
3. The numbers have rubbed off your CD 4017 and CD 4001 IC's. Using only a multimeter, how can you find the CD 4001?
4. A 555 oscillator is running too fast. Would you increase the value of C?
5. What is a "pull-up" resistor?
6. List 4 NEW items learnt from this issue:

LIGHT THE LED
CD 4017
CD 4001
SW
LED ZEPPELIN
8 5 1 4
14 8 1 7
TALKING
16 9 1 8
ELECTRONICS
EXPERIMENTER
CD 4001
CD 4017
DECK No1
7 Segment
Display
com
dp
AND 4145
Counter
74C926

DATA

CAPACITOR:

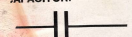

mfd = microfarad
pf = picofarad
n = nanofarad

1000pf = 1n
1n = .001 mfd
1000n = 1 mfd
2n2 = .0022 mfd
22n = .022 mfd
220n = .22 mfd

102 = 1,000pf
103 = 10,000pf
= .01 mfd
104 = .1 mfd
105 = 1 mfd

472 = .0047 = 4n7
473 = .047 = 47n
474 = .47 = 470n

DIODE:

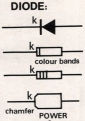

TRANSFORMER:

BC 547 NPN SI

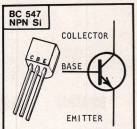

BC 557 PNP SI

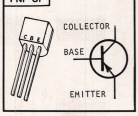

IC PIN NUMBERS:

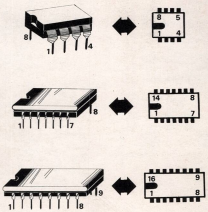

USING A MULTIMETER TO FIND PNP or NPN:

1. Clip meter -ve lead onto centre lead of transistor.
2. Set multimeter to high ohms (x1k range)
3. Positive lead to outer pins reads:
   HIGH-HIGH IT's PNP
   LOW-LOW IT's NPN

If "b" unknown - use transistor tester on Page 27 of issue No1.

7-SEGMENT DISPLAY

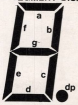

WIRING DISPLAYS:

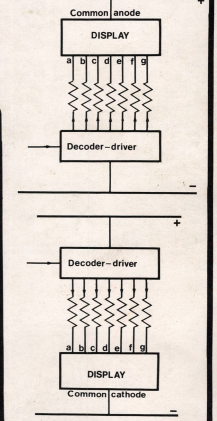

PIN OUTS:

CD 4001

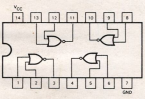

CD 4011

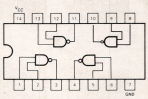

CD 4017

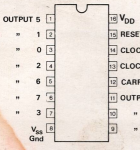

555

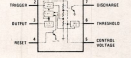

Gates:

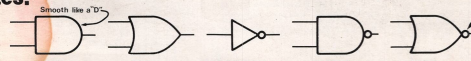

CPW